

# Principles of Physics II (PHY112)

## Lab

### Experiment no: 6

**Name of the experiment:** Determination of the ratio of the electromotive forces of two cells by using a potentiometer

#### Theory

Electromotive force of a cell is the amount of work performed by the cell to move one unit of positive charge (1 C, is SI unit), starting from a point of a circuit, through the whole circuit, and then bring it back to the starting point. We measure electromotive ('emf') force of a circuit in the unit of Volts (V). In this experiment we are going to measure the ratio of electromotive forces of two given cells. If the emf of a cell is known to us, then we can determine the emf of other one.

#### Potentiometer

Potentiometer is a device to measure potential difference and electromotive force. In this device a wire of 10 m length and uniform cross section is attached with a wooden frame. The wire has significant resistance. It has 10 segments. Each of the segments is of 1 m length. The segments are connected with each other in a series combination. The wire consists of a material, whose thermal coefficient of resistance is low, i.e., its specific resistance does not change much with the change of temperature. Usually, Manganin or Constantan is used.

By using a potentiometer the electric potential difference ("voltage difference") across a component can be determined by applying the principle of a *potential divider*.

#### Potential Divider

Figure 1 shows a simple potential divider. Two resistors of resistances  $R_1$ ,  $R_2$  and a voltage source of electromotive force  $E$  are connected in series combination. Total  $I$  amount of current is passing through the closed loop. Voltage differences across the resistance  $R_1$  and  $R_2$  are  $V_1$  and  $V_2$  respectively. Therefore, according to Kirchhoff's law,  $E = V_1 + V_2$

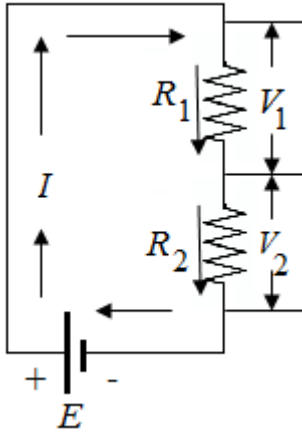


Figure 1: A simple potential divider

According to Ohm's law,  $V_1 = I R_1$  &  $V_2 = I R_2$

$$\text{Therefore, } E = I R_1 + I R_2 = I (R_1 + R_2) \Rightarrow I = \frac{E}{(R_1 + R_2)}$$

Finally, we get rule of potential division between two resistors connected in series combination,

$$\boxed{\begin{aligned} V_1 &= \frac{R_1}{(R_1 + R_2)} E \\ V_2 &= \frac{R_2}{(R_1 + R_2)} E \end{aligned}} \quad (1)$$

A conductor of uniform cross section and having significant resistance connected with a cell can serve as a potential divider, as shown in the Figure 2. The rheostat  $R_h$  is used to modulate the total current,  $I$ . A and B are the two ends of this conductor. A terminal is connected with the circuit at point A. Another terminal comes out from point J. We can slide it along the conductor. We get an output voltage difference of  $V_{out}$  between the A and J terminal. The resistances of the conductor's segments AJ and JB are  $R_{AJ}$  and  $R_{JB}$  respectively. Total resistance of the conductor,  $R = R_{AJ} + R_{JB}$ . Suppose, the length of the conductor is  $L$  and the length of the AJ segment is  $l$ . Since, the conductor has uniform cross section; the resistance of any of its segment is proportional to the length of that segment. If  $\sigma$  is the resistance per unit length of the conductor then  $R_{AJ} = l\sigma$  and  $R = L\sigma$ . According to the potential division rule:

$$\begin{aligned} V_{out} &= \frac{R_{AJ}}{R_{AJ} + (R_{JB} + R_h)} E = \frac{R_{AJ}}{R + R_h} E = \frac{l\sigma}{L\sigma + R_h} E = \frac{E}{L + R_h / \sigma} l \\ \Rightarrow \boxed{V_{out} &= \frac{E}{L + R_h / \sigma} l} \end{aligned} \quad (2)$$

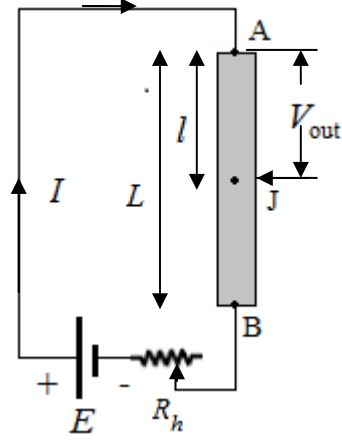


Figure 2: A conductor AB having uniform cross section connected with a cell in series serving as a potential divider.

Let us connect a series combination of a cell of emf  $E_1$  and a galvanometer  $G$  with the output terminals A and J (figure 3). **The positive electrodes of  $E_1$  and  $E$  are connected with a same node, A.** The resistance  $R_o$  is the combined resistance of the galvanometer and the internal resistance of the cell,  $E_1$ . After reaching the junction A the current  $I$  gets divided into two flows:  $I_G$  and  $I_C$ .  $I_G$  passes through the  $E_1$ ,  $R_o$  and  $G$ . On the other hand,  $I_C$  passes through the AJ segment of the conductor. According to Kirchhoff's current rule:  $I = I_G + I_C$ . Voltages at nodes A, C and J are  $V_A$ ,  $V_C$  and  $V_J$  respectively.

$I_G$  amount of current passes through the resistance  $R_o$ . According to Ohm's law,

$$V_C - V_J = I_G R_o \quad (3)$$

Voltage difference across  $E_1$ ,

$$V_A - V_C = E_1 \quad (4)$$

By summing equations (3) and (4) we get,

$$V_A - V_J = E_1 + I_G R_o \quad (5)$$

However, that is the output voltage difference between terminals A and J provided by the potential divider. Hence, according to the equation (2) we can write,

$$\begin{aligned} \frac{E}{L + R_h / \sigma} l &= E_1 + I_G R_o \\ \Rightarrow \frac{E}{L + R_h / \sigma} l - E_1 &= I_G R_o \\ \Rightarrow I_G &= \frac{1}{R_o} \left[ \frac{E}{L + R_h / \sigma} l - E_1 \right] \end{aligned} \quad (6)$$

$I_G$  can be positive or negative depending on the parameters which appear inside the square brackets of the right hand side of equation (6).

In Figure 3, both of the positive electrodes of  $E$  and  $E_1$  are connected with A. However, instead of that if the negative electrode of  $E$  and the positive electrode of  $E_1$  were connected with the junction A, then in equation (6),  $E$  would be negative and  $E_1$  would be positive. Eventually,  $I_G$  would be always negative. That means current would always pass through the  $E_1$  &  $G$  opposite to our presumed direction as shown in the Figure 3, i.e., it would flow from C to A, instead of from A to C.

Again, if the positive electrode of  $E$  and the negative electrode of  $E_1$  were connected with the junction A then in equation (6),  $E$  would be positive and  $E_1$  would be negative. Therefore  $I_G$  would be always positive. That means current would always pass through the  $E_1$  &  $G$  towards our presumed direction as shown in the Figure 3, i.e., it would flow from A to C.

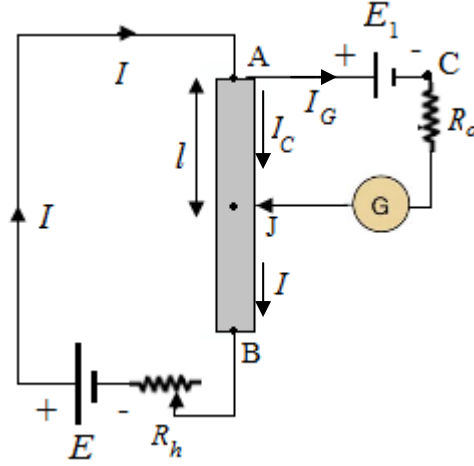


Figure 3: The output terminals A & J of the conductor AB of figure 5 are now connected with a cell of  $E_1$  emf and a galvanometer,  $G$ .  $E_1$  and  $G$  are in series combination. The resistance  $R_o$  is the combined resistance of the galvanometer and the internal resistance of the cell,  $E_1$ .

If both of  $E$  and  $E_1$  are either positive or negative then depending on  $l$ ,  $I_G$  can be either negative or positive, i.e., the current through G can either flow from C to J or from J to C. Therefore, to make sure that the galvanometer's pointer can deflect towards both sides, the first condition is polarity of the electrodes of  $E$  and  $E_1$  should be same which are connected with the junction A.

Suppose, both  $E$  and  $E_1$  are connected as shown in Figure 3. If we slide the terminal J and keep it near A, then  $l$  will be sufficiently small and according to equation (6) the magnitude of the current  $I_G$  will be negative. Then the current  $I_G$  will actually flow toward the opposite to its presumed direction as shown in Figure 3. If we slide the terminal J and keep it near B, then  $l$  will be sufficiently bigger and according to equation (6) the magnitude of the current  $I_G$  may be positive. Then the current  $I_G$  will flow toward the direction as shown in the Figure 3. Depending on the position of J, direction & amount of the current passing through the galvanometer will be different and the galvanometer's pointer will deflect accordingly.

To observe galvanometer's pointer can deflect towards both directions, depending on the value of  $l$ ,  $I_G$  should be either positive or negative. When  $l$  is zero then clearly,  $I_G (= -E_1/R_0)$  is negative. However, the maximum value of  $l$  can be  $L$ . So, to get  $I_G$  positive,

$$\frac{E}{L + R_h / \sigma} L - E_1 > 0 \Rightarrow \frac{1}{L + R_h / \sigma} > \frac{E_1}{LE} \Rightarrow L + R_h / \sigma < \frac{LE}{E_1} \Rightarrow R_h < \frac{\sigma LE}{E_1} - L\sigma$$

$$\Rightarrow R_h < R \frac{(E - E_1)}{E_1} \text{ [Since, } L\sigma = R \text{]}$$

Therefore, to get the galvanometer's pointer to deflect towards both directions, depending on the position of J, the value of the rheostat should be lower than this cut off value  $R \frac{(E - E_1)}{E_1}$ .

For a particular position of J on the conductor AB, no current will pass through the galvanometer, i.e.,  $I_G = 0$ . This is called '*null point*'. The pointer of the galvanometer will not deflect. If  $I_G = 0$  then from equation (6) we get,

$$E_1 = \frac{E}{L + R_h / \sigma} l$$

Here,  $l$  is the length of the segment of the conductor between the *null point* and the end A of the conductor where the electrodes of same polarity (in our example, positive electrodes) of  $E$  and  $E_1$  are connected. Let's put a subscript 1 under  $l$  to denote that this corresponds to  $E_1$ .

$$E_1 = \frac{E}{L + R_h / \sigma} l_1$$

(7)

Suppose, now we connect a cell of emf  $E_2$  instead of cell  $E_1$ . Now, the length of the segment of AB is found  $l_2$  distance away from A. Therefore,

$$E_2 = \frac{E}{L + R_h / \sigma} l_2 \quad (8)$$

If we divide equation (7) by equation (8) then we get,

$$\boxed{\frac{E_1}{E_2} = \frac{l_1}{l_2}} \quad (9)$$

By using this equation we can compare two voltages, using a potentiometer.

### Circuit Construction

A potentiometer works as a potential divider. The schematic diagram of the circuit construction of this experiment is shown below (Figure 4):

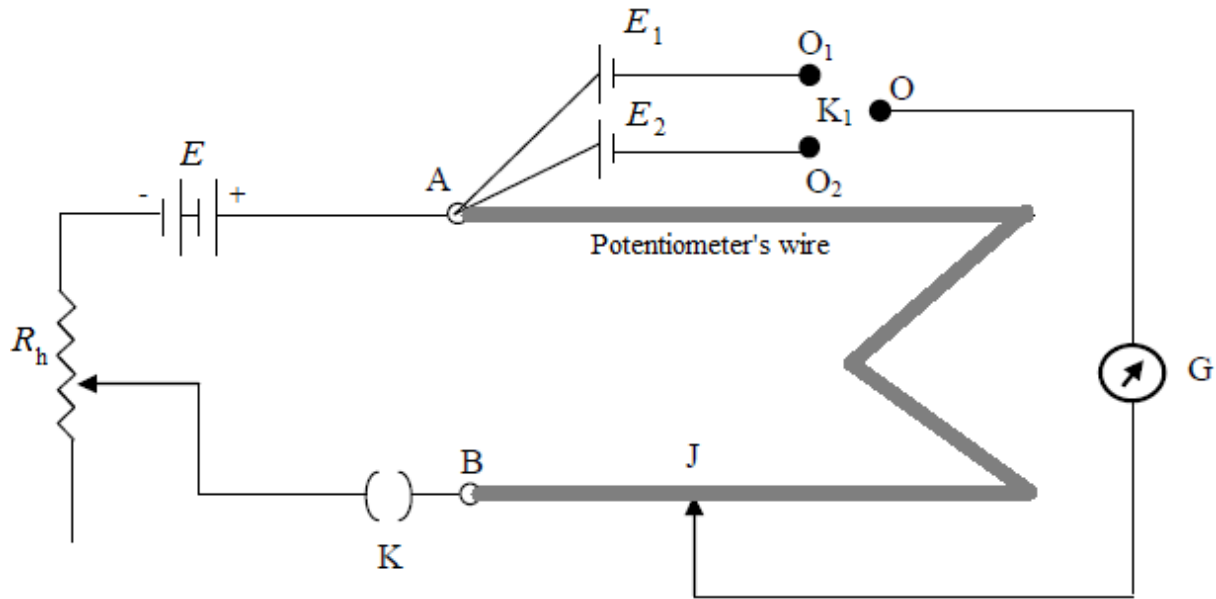


Figure 4: Schematic diagram of the circuit construction to determine the ratio of electromotive forces of two cells by using a potentiometer

Compare this circuit construction with Figure 3. The potentiometer's wire, which has a significant resistance, plays the role of the conductor AB.  $K_1$  is a 'single pole double throw' switch. Positive electrodes of the cells ( $E_1$  and  $E_2$ ) and the DC voltage source  $E$ , are connected with end A of the potentiometer's wire. Negative electrodes of  $E_1$  and  $E_2$  are connected with the throws  $O_1$  and  $O_2$ , of the switch  $K_1$ , respectively. The pole O is connected with one terminal of a Galvanometer, G. Other terminal of the galvanometer is connected with a jockey. The point of contact between the jockey and the potentiometer's wire is J. The negative electrode of  $E$  is connected with one end of a Rheostat. Other end

of the rheostat is connected with a key, K. The key K is connected with the end B of the potentiometer's wire.

When O & O<sub>1</sub> are connected then E<sub>1</sub> is connected with the galvanometer in series combination and E<sub>2</sub> remains disconnected. We find the null point on the potentiometer's wire, measure the length,  $l_1$  of the wire's segment between end A and the null point. Similarly, when O & O<sub>2</sub> are connected then E<sub>2</sub> is connected with the galvanometer in series combination and E<sub>1</sub> remains disconnected. Then we find the null point and the length,  $l_2$  of the wire's segment between end A and the null point which correspond to E<sub>2</sub> in the same way.

Finally, we work out the ratio of the electromotive forces of the two given cells using equation (9).

### **Potentiometer as an electromotive force measuring device**

We can measure the voltage of a cell by using a voltmeter or a digital multi-meter. However, to cause the deflection of the voltmeter's pointer or to cause an electric impulse in the digital multi-meter, a tiny amount of current should be allowed to flow through the voltmeter's coil or the multi-meter's internal circuit. That will certainly cause a potential drop between the two electrodes of the cell, since that amount of current will also flow through the electrolyte(s), inside the cell between its two electrodes. This current inside the cell has to overcome the cell's internal resistance which results the little potential drop. That is why what we observe in a voltmeter or a digital multi-meter when we measure the electromotive force of a cell, is slightly lower than its actual value. On the other hand, when we use the potentiometer to measure the cell's electromotive force, no current passes through the galvanometer assuring that no current passes through the cell (connected in series combination with the galvanometer), as well. Hence no potential drop occurs across the internal resistance of the cell. This is an advantage of a potentiometer as a measuring device of electromotive force.

However, to make the assumption that- 'resistance of a certain portion of the potentiometer's wire is proportional to its length'; the cross sectional area of this wire should be same everywhere. Left and right ends of every segment of the wire should coincides with the 0 and 100cm marks of the meter-scale respectively, otherwise an 'end correction' should be made. Connections of the wires should be tight. Weak connections may cause the fluctuations of the galvanometer's pointer. Voltage of the DC voltage source,  $E$  should be same while taking the measurement of  $l_1$  and  $l_2$ . When current passes through the wire, it will increase its temperature. Resistance of a body changes with temperature. The potentiometer's wire should consist of a material whose thermal coefficient of resistance is very low, so that the resistance of the wire will not change much due to the change of the temperature.

### **Apparatus**

A potentiometer, a DC voltage source, two cells, a rheostat, a 'single pole double throw' switch, a 'single pole single throw' switch, a galvanometer, copper wires (of insignificant resistance).

### **Procedure**

1. Construct the circuit as shown in the Figure 4. Make sure that the galvanometer's pointer deflects towards opposite directions when you make contact between the jockey and the potentiometer's

wire near end A and end B. Do it for both cells when they are connected with the galvanometer separately.

2. Connect O and  $O_1$ . Cell  $E_1$  is connected with the galvanometer. Find out the null point. Record the length of the wire-segment between end-A and the null point, i.e.,  $l_1$ .
3. Connect O and  $O_2$ . Cell  $E_2$  is connected with the galvanometer. Find out the null point. Record the length of the wire-segment between end-A and the null point, i.e.,  $l_2$ .
4. Find out  $E_1/E_2$  ( $=l_1/l_2$ ).
5. Slightly change the resistance of the rheostat. Repeat the steps 2-4.
6. Repeat step 5 for 4 times.
7. Finally work out the average of  $E_1/E_2$ .

**Read carefully and follow the following instructions:**

- Please **READ** the theory carefully, **TAKE** printout of the ‘Questions on Theory’ and **ANSWER** the questions in the specified space **BEFORE** you go to the lab class.
- To get full marks for the ‘Questions on Theory’ portion, you must answer **ALL** of these questions **CORRECTLY** and with **PROPER UNDERSTANDING**, **BEFORE** you go to the lab class. However, to **ATTEND** the lab class you are **REQUIRED** to answer **AT LEAST** the questions with asterisk mark.
- Write down your **NAME, ID, THEORY SECTION, GROUP, DATE, EXPERIMENT NO AND NAME OF THE EXPERIMENT** on the top of the first paper.
- If you face difficulties to understand the theory, please meet us **BEFORE** the lab class. However, you must read the theory first.
- **DO NOT PLAGIARIZE.** Plagiarism will bring **ZERO** marks in this **WHOLE EXPERIMENT**. Be sure that you have understood the questions and the answers what you have written, and all of these are your own works. You **WILL BE** asked questions on these tasks in the class. If you plagiarize for more than once, **WHOLE** lab marks will be **ZERO**.
- After entering the class, please submit this portion before you start the experiment.

**Name:** \_\_\_\_\_ **ID:** \_\_\_\_\_ **Sec:** \_\_\_\_ **Group:** \_\_ **Date:** \_\_\_\_\_

**Experiment no:** \_\_\_\_

**Name of the Experiment:** \_\_\_\_\_

\_\_\_\_\_

**Questions on theory (all diagrams should be drawn by using a pencil and a scale)**

\*1) What is electromotive force of a cell? [0.25]

Ans:

\*2) See Figure 1. Draw it and work out the rule of voltage division for this circuit. [0.25]

Ans:



\*3) See Figure 2. Draw it and work out an expression of  $V_{\text{out}}$  in terms of  $E$ ,  $l$ ,  $L$ ,  $R$ ,  $R_h$  and  $\sigma$ .  $\sigma$  is the resistance per unit length of the conductor AB.  $R$  is the total resistance of the conductor. [1]

Ans:

\*4) See Figure 3. Draw it and work out an expression of the current passing through the galvanometer,  $I_G$  as shown in equation (6). [2]

Ans:

\*5) When  $I_G$  is zero, then show that,  $E_1 = \frac{E}{L + R_h / \sigma} l$  [0.25]

Ans:

\*6) If  $l_1$  and  $l_2$  are the length of the segment of the potentiometer's wire and the null point, correspond to  $E_1$  and  $E_2$ , then show that  $\frac{E_1}{E_2} = \frac{l_1}{l_2}$  [0.25]

Ans:

\*7) Draw the schematic diagram of the circuit construction to determine the ratio of the electromotive forces of two given cells by using a potentiometer. [0.5]

8) See the Figure 5 which shows the circuit construction to compare the emf of two cells with a potentiometer. When  $OO_1$  is connected then the null point of the galvanometer is found at  $J_1$ . When  $OO_2$  is connected then the null point of the galvanometer is found at  $J_2$ . What is the approximate value of  $\frac{E_1}{E_2}$  ?  
[0.5]

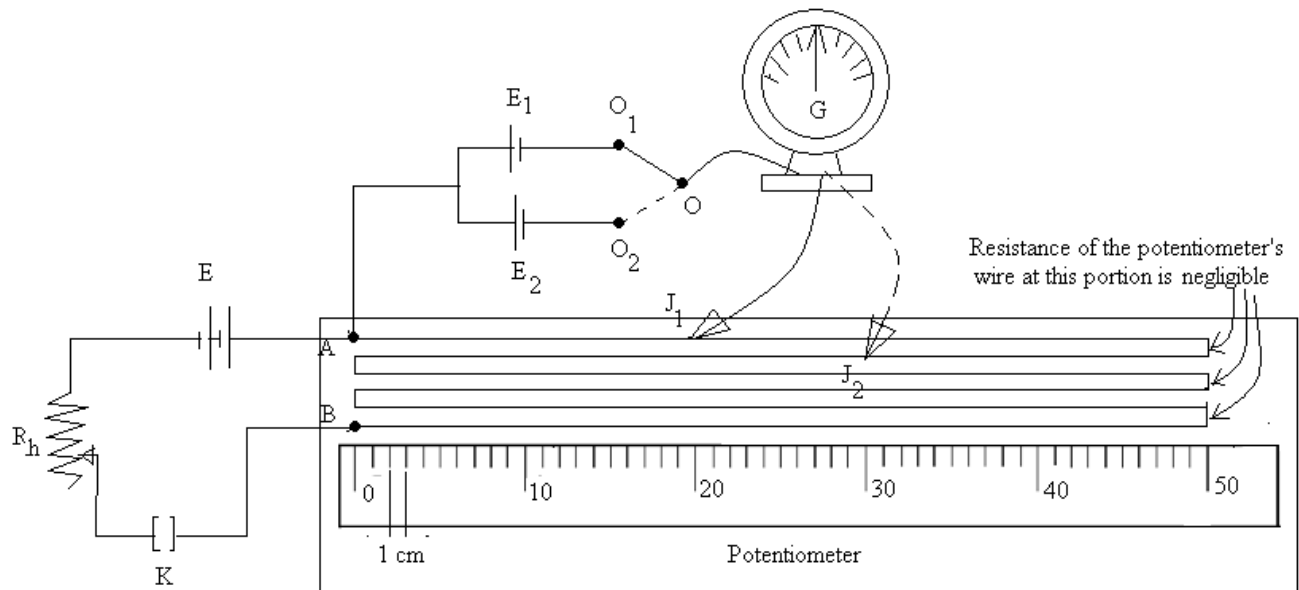


Figure 5: Figure for question 8

Ans:

- Draw the data table(s) and write down the variables to be measured shown below (in the ‘Data’ section), using pencil and ruler BEFORE you go to the lab class.
- Write down your NAME and ID on the top of the page.
- This part should be separated from your Answers of “Questions on Theory” part.
- Keep it with yourself after coming to the lab.

## Data

Table: Data for calculating the ratio of emf of two cells

No. of obs.	Cell	Null points			Total length (cm)	$E_1/E_2 = l_1/l_2$	Mean $E_1/E_2$
		Wire - segment number	Scale reading (cm)	Mean scale reading (cm)			
1	First (E <sub>1</sub> )						
	Second (E <sub>2</sub> )						
2	First (E <sub>1</sub> )						
	Second (E <sub>2</sub> )						
3	First (E <sub>1</sub> )						
	Second (E <sub>2</sub> )						
4	First (E <sub>1</sub> )						
	Second (E <sub>2</sub> )						
etc.							

- READ the PROCEDURE carefully and perform the experiment by YOURSELVES. If you need help to understand any specific point draw attention of the instructors.
- DO NOT PLAGIARIZE data from other group and/or DO NOT hand in your data to other group. It will bring ZERO mark in this experiment. Repetition of such activities will bring zero mark for the whole lab.
- Perform calculations by following the PROCEDURE . Show every step in the Calculations section.
- Write down the final result(s)

## Calculations

## Results

- **TAKE printout of the ‘Questions for Discussions’ BEFORE you go to the lab class. Keep this printout with you during the experiment. ANSWER the questions in the specified space AFTER you have performed the experiment.**
- **Attach Data, Calculations, Results and the Answers of ‘Questions for Discussions’ parts to your previously submitted Answers of ‘Questions on Theory’ part to make the whole lab report.**
- **Finally, submit the lab report before you leave the lab.**

Name: \_\_\_\_\_ ID: \_\_\_\_\_

**Questions for Discussions**

- 1) If you see the galvanometer's pointer always deflects towards same direction when you make the contact between the jockey and the wire, near end A and end B; what might be the possible reason(s) for this? [0. 5]

Ans:


- 2) We can use a voltmeter or a multi-meter to measure the emf of a cell. What might be a drawback of using a voltmeter or a multi-meter for this purpose? How can a potentiometer be useful to avoid this drawback? [0.5]

Ans:

- 3) The Figure 6 shows a typical single turn potentiometer, but its structure is quite different from the potentiometer which you have used in the lab. You can see three terminals, and a knob which can be rotated. In the right side, you see its internal structure. The grey colored circular object is a conductor of significant resistance having uniform thickness. Yellow colored object is a good conductor whose resistance can be neglected, an L shaped portion of which touches the circular conductor at a point J as shown in the Figure 6. By rotating the knob we can slide this L shaped portion around the circular conductor. Explain how you can use this single turn potentiometer as a potential divider. [1]



(a) External view

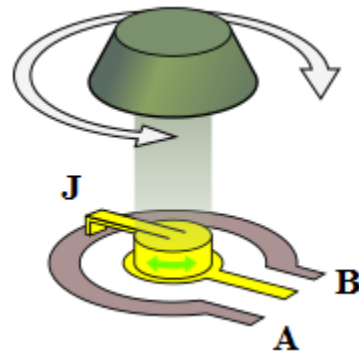

(b) Internal structure

Figure 6: Single turn potentiometer (Courtesy: Wikimedia)

Ans:

**NOTE: Some of the figures shown in this lab manual are collected from internet. They are free from copyright or the copyright holders grant permission to use them.**

<https://commons.wikimedia.org/wiki/File:Potentiometer.jpg>

[https://commons.wikimedia.org/wiki/File:Potentiometer\\_diagram.svg](https://commons.wikimedia.org/wiki/File:Potentiometer_diagram.svg)