

CSE-250

Assignment - 01

Name: MD Ikramul Kayes


ID : 21301576

Sec : 07

Slide-3

Problem 5

Ans:

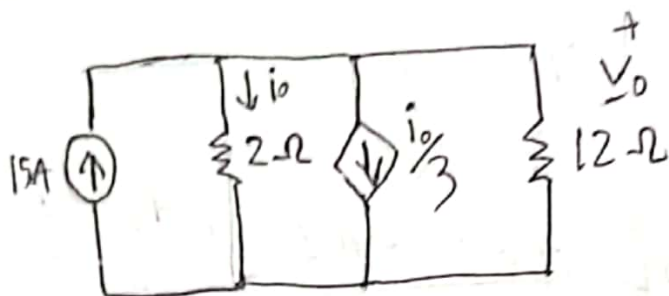

We can write from the circuit that,

$$15 = i_o + \frac{i_o}{3} + \frac{V_o}{12}$$

$$\Rightarrow 15 = \frac{4}{3} i_o + \frac{V_o}{12} \quad \text{--- (1)}$$

in the equation,

$$V_o = 2i_o$$

$$\therefore 2i_o - V_o = 0 \quad \text{--- (2)}$$

Solving eq (1) and (2) we get,


$$i_o = 10 \text{ A}$$

$$V_o = 20 \text{ V}$$

(Ans)

Slide = 3

Problem 6

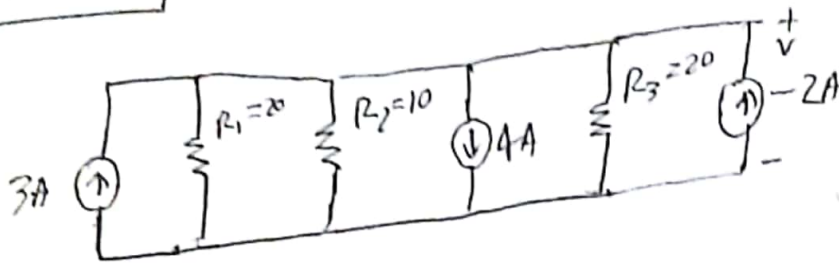

Here,

$$\frac{1}{R_{12}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{20} + \frac{1}{10}$$

$$\Rightarrow R_{12} = \frac{20}{3} \Omega$$

Again,


$$\frac{1}{R_{123}} = \frac{1}{R_{12}} + \frac{1}{R_3}$$

$$= \frac{3}{20} + \frac{1}{20}$$

$$\Rightarrow R_{123} = 5 \Omega$$

Net electricity flow in the circuit,
is $3A - 4A - 2A = -3A \leftarrow$ means down-ward

So, the circuit can be drawn now as,

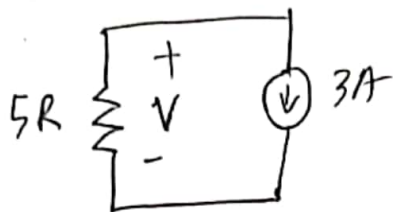

$$V = -3 \times 5 \\ = -15V$$


For getting the I we need to count the ~~next~~ net electricity flow of the right portion of the circuit.

Here, supplied current I equivalent to,

$$\begin{aligned} \cancel{I} &= \cancel{4A} - \frac{R_3}{R_3} + 2A \\ I &= 4A - \frac{15}{R_3} + 2A \\ \Rightarrow I &= 4 - \frac{15}{20} + 2 \\ &= 5.25A \end{aligned}$$

slide -3

Problem - 7

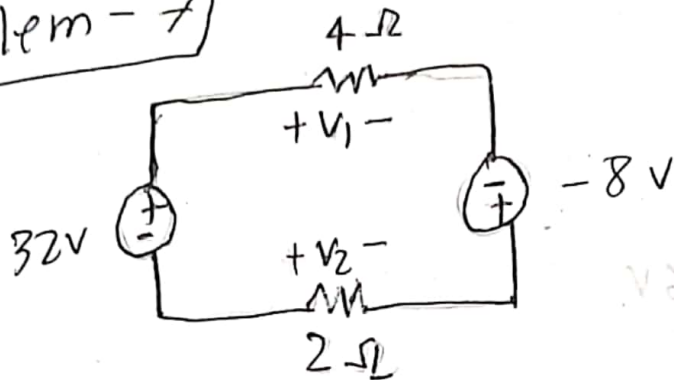

From the circuit we can write the KVL equation $\rightarrow -32 + 4i + 8 + 2i = 0$

$$\Rightarrow 6i = 24$$

$$\therefore i = 4A$$

$$\text{Now, } V_1 = + (4 \times 4)$$


$$= 16V$$

$$V_2 = \cancel{-(2 \times 4)} - (2 \times 4)$$

$$= -8V$$

Slide-3

Problem 8

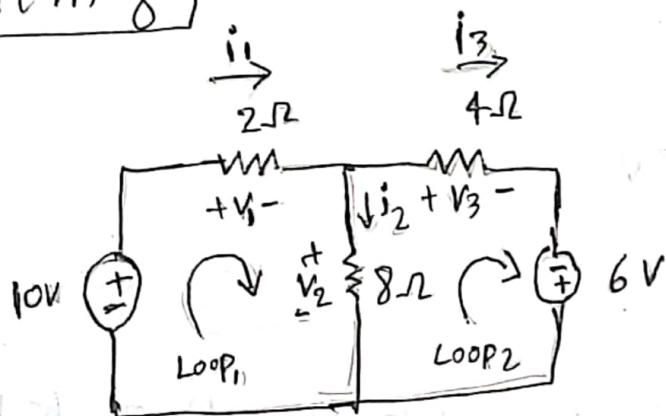

From the circuit we get KVL for the First Loop

$$\Rightarrow -10 + 2i_1 + 8i_2 = 0 \quad \text{--- (1)}$$

we get for the second Loop

$$\Rightarrow 4i_3 - 6 - 8i_2 = 0 \quad \text{--- (2)}$$

As we can say from the circuit

$$\text{that, } i_1 = i_2 + i_3$$

∴ equation ① will be,

$$-10 + 2(i_2 + i_3) + 8i_2 = 0$$

$$\Rightarrow -10 + 2i_3 + 10i_2 = 0 \quad \text{--- (11)}$$

By solving equation ⑪ and ⑩ we get,


$$i_2 = \frac{1}{2} A$$

$$i_3 = \frac{5}{2} A$$

$$i_1 = i_2 + i_3 = \frac{1}{2} + \frac{5}{2} = 3A$$

Slide 3

Problem 9

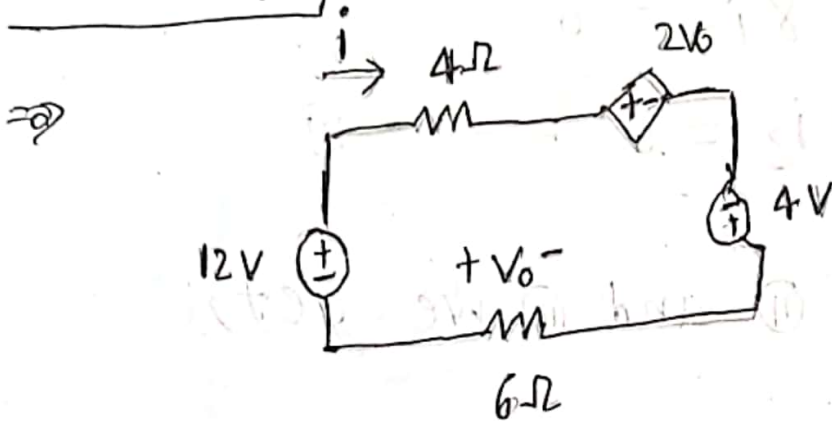

we get the KVL equation for the circuit

$$\Rightarrow -12 + 4i + 2V_o - 4 + 6i = 0$$

$$\Rightarrow 10i - 16 + 2V_o = 0$$

$$\Rightarrow i = \frac{16 - 2V_o}{10}$$

From the circuit we can also write,

$$\Rightarrow -V_o = i \times 6$$

$$\Rightarrow -V_o = \frac{16 - 2V_o}{10} \times 6$$

$$\Rightarrow -V_o \times \frac{5}{3} = 16 - 2V_o$$

$$\Rightarrow \frac{1}{3} V_0 = 16$$

$$\therefore V_0 = 16 \times 3 \\ = 48 \text{ V}$$


Again,

$$6i = -48 \text{ A} \quad [-V_0 = 6i]$$

$$\Rightarrow i = -8 \text{ A}$$

slide-3

Problem-10

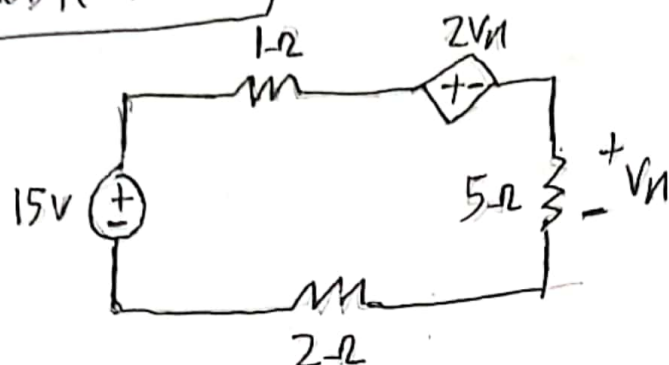

We can write the KVL equation for the circuit,

$$\Rightarrow -15 + i + 2V_H + 5i + 2i = 0$$

$$\Rightarrow 8i = 15 - 2V_H$$

$$\Rightarrow i = \frac{15 - 2V_H}{8} \quad \text{--- (1)}$$

From the circuit we can also write,

$$\Rightarrow V_H = iR$$

$$\Rightarrow V_H = \frac{15 - 2V_H}{8} \times 5 \quad [\text{From eq (1)}]$$

$$\Rightarrow \frac{8}{5} V_H = 15 - 2V_H$$

$$\Rightarrow \frac{18}{5} V_H = 15$$


$$\Rightarrow V_H = \frac{5}{18} \times 15$$

$$= 4.167 \text{ V}$$

(Ans)

Slide - 3

Problem 11

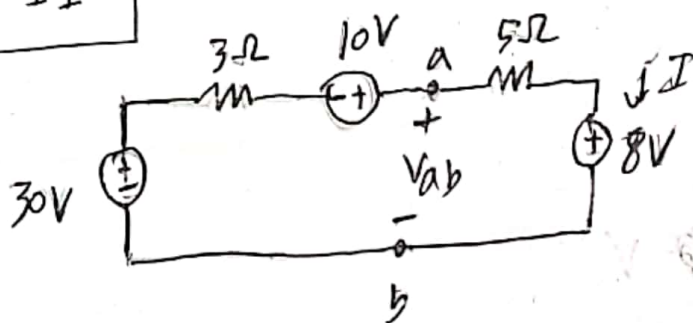

From the equation we can write the KVL equation,

$$\Rightarrow -30 + 3i - 10 + 5i + 8 = 0 \quad \text{--- (1)}$$

$$\Rightarrow 8i = 48$$

$$\therefore i = 4A$$

We can modify the eq (1) into,


$$\Rightarrow -30 + 3i - 10 + V_{ab} = 0$$

$$\Rightarrow -30 + 3 \times 4 - 10 + V_{ab} = 0 \quad [i = 4A]$$

$$\Rightarrow V_{ab} = 28V \quad (\text{Ans})$$

Slide-4

Problem 3

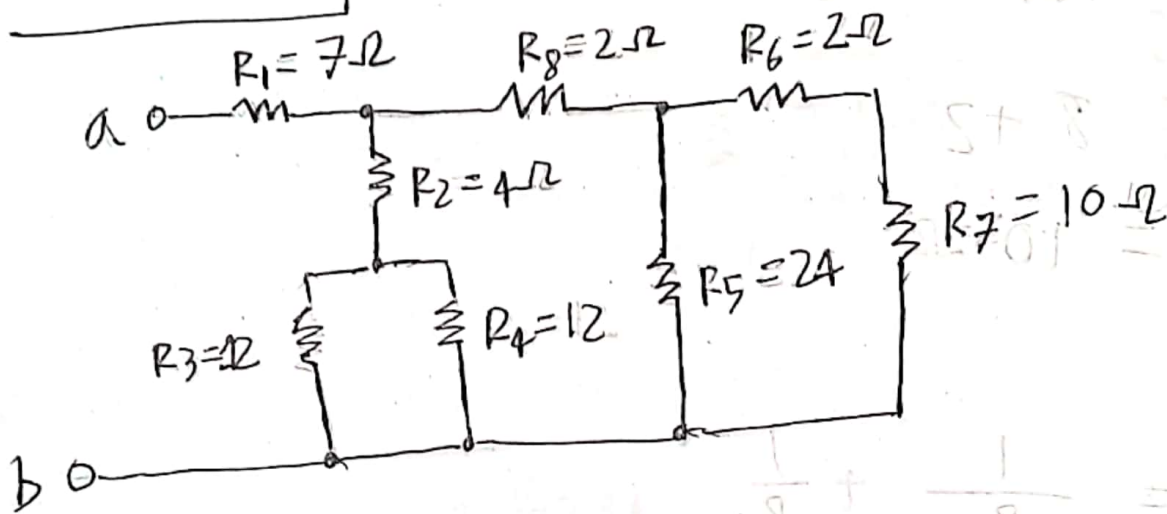

From the circuit we can write

$$R_{67} = R_6 + R_7 = 2 + 10 = 12\Omega$$

~~R_{567}~~ Also,

$$\begin{aligned}\frac{1}{R_{567}} &= \frac{1}{R_5} + \frac{1}{R_{67}} \\ &= \frac{1}{24} + \frac{1}{12}\end{aligned}$$


$$\therefore R_{567} = 8\Omega$$

$$R_{2567} =$$

$$R_{5678} = R_{567} + R_8$$

$$= 8 + 2$$

$$= 10 \Omega$$

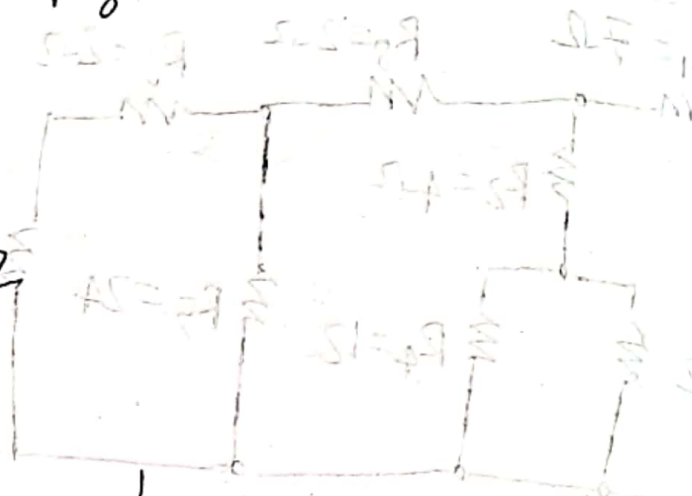


Also,

$$\frac{1}{R_{34}} = \frac{1}{R_3} + \frac{1}{R_4}$$

$$\Omega = \frac{1}{12} + \frac{1}{12}$$

$$= 6 \Omega$$

Now the circuit looks,

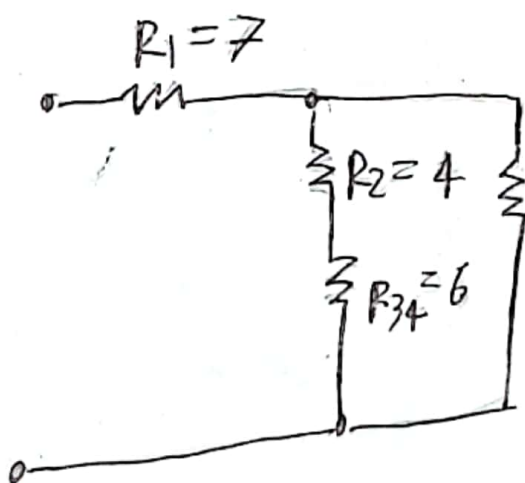

$$R_{5678} = 10$$

$$R_{234} = R_2 + R_{34} = 4 + 6 = 10 \Omega$$

Now,

$$\frac{1}{R_{234567}} = \frac{1}{R_{234}} + \frac{1}{R_{5678}}$$

$$\Rightarrow \frac{1}{R_{234567}} = \frac{1}{10} + \frac{1}{10}$$

$$\therefore R_{234567} = 5 \Omega$$


Now, $R_{ab} = R_1 + R_{234567}$

$$= 7 + 5$$

$$= 12 \Omega$$

Slide 4

Problem 4

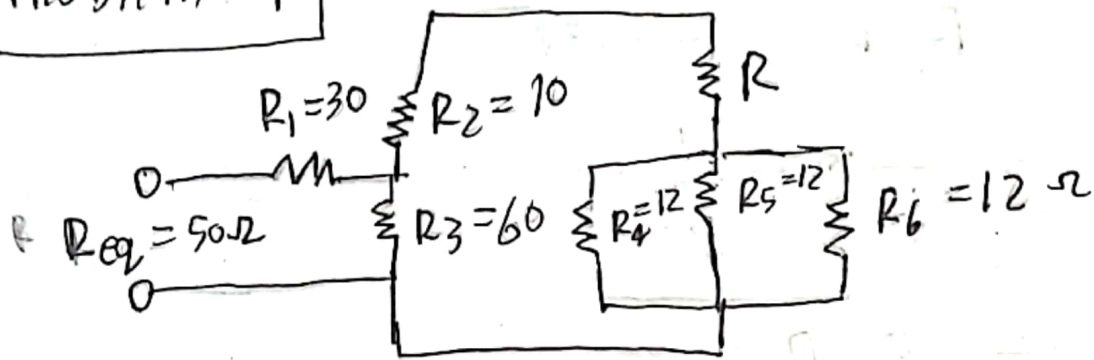

From the circuit we can write,

$$\frac{1}{R_{456}} = \frac{1}{R_4} + \frac{1}{R_5} + \frac{1}{R_6}$$

$$\Rightarrow \frac{1}{R_{456}} = \frac{1}{12} + \frac{1}{12} + \frac{1}{12}$$

$$\therefore R_{456} = \cancel{3} 4 \Omega$$


Now,

$$R + R_{456} = \cancel{R} R + 4$$


Also,

$$\begin{aligned} R + R_{2456} &= R + 4 + 10 \\ &= R + 14 \end{aligned}$$

Circuit now,

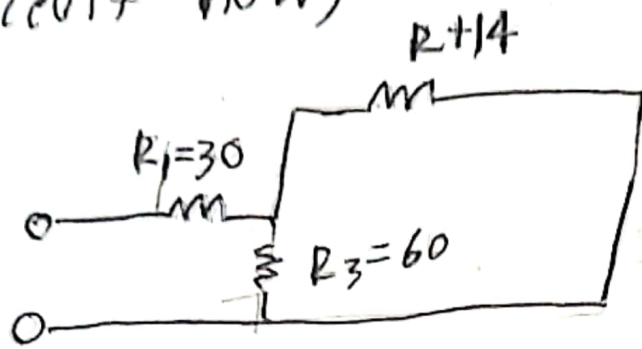

Now, we can write the equation,

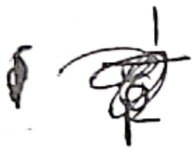

$$\left(\frac{1}{R+14} + \frac{1}{60} \right)^{-1} + 30 = 50$$


$$\Rightarrow \frac{1}{R+14} + \frac{1}{60} = \frac{1}{20}$$

$$\Rightarrow \frac{1}{R+14} = \frac{1}{30}$$


$$\Rightarrow R+14 = 30$$

$$\therefore R = 16 \Omega$$

(Ans)

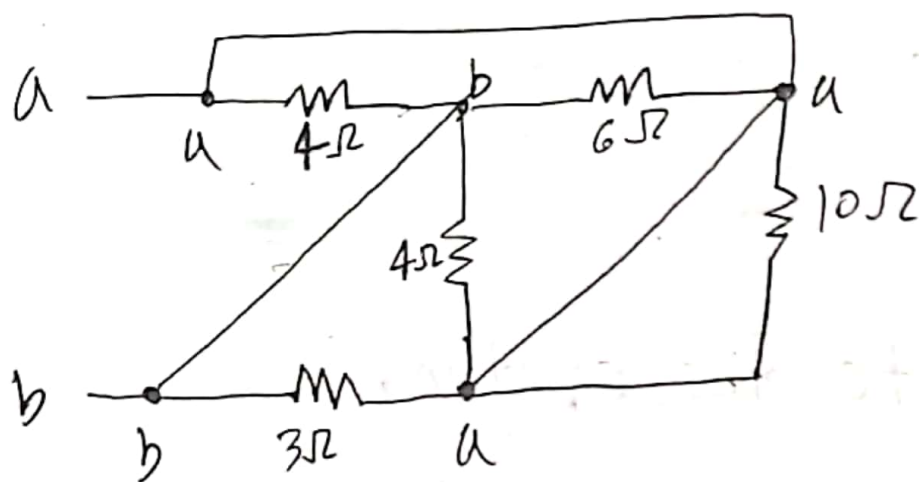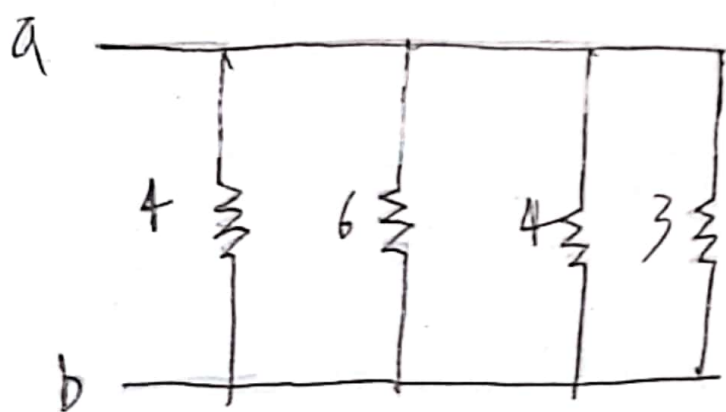Problem 5Slide - 4

~~As the whole circuit~~
As the whole circuit have only two nodes we can draw the circuit in the following manner,



As 10Ω resistance is not included in the new circuit because of the


Short wire,

$$\therefore \frac{1}{R_{ab}} = \frac{1}{4} + \frac{1}{6} + \frac{1}{4} + \frac{1}{3}$$

$$\therefore R_{ab} = 1 \Omega \quad (\text{Ans})$$

Slide - 4

Problem 6)

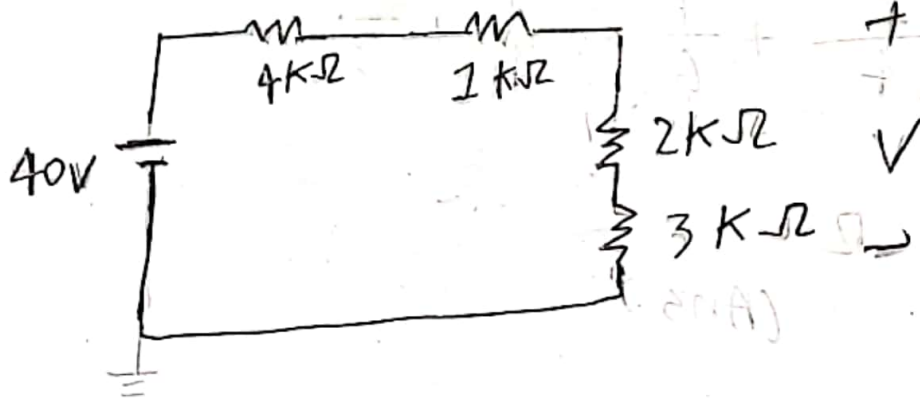

we can write the circuit as,



~~we~~ If we use voltage division rule we get,


$$V = \frac{5k\Omega}{5k\Omega + 5k\Omega} \times 40V$$

$$= 20V$$


(Ans)

Slide - #

Problem - 7

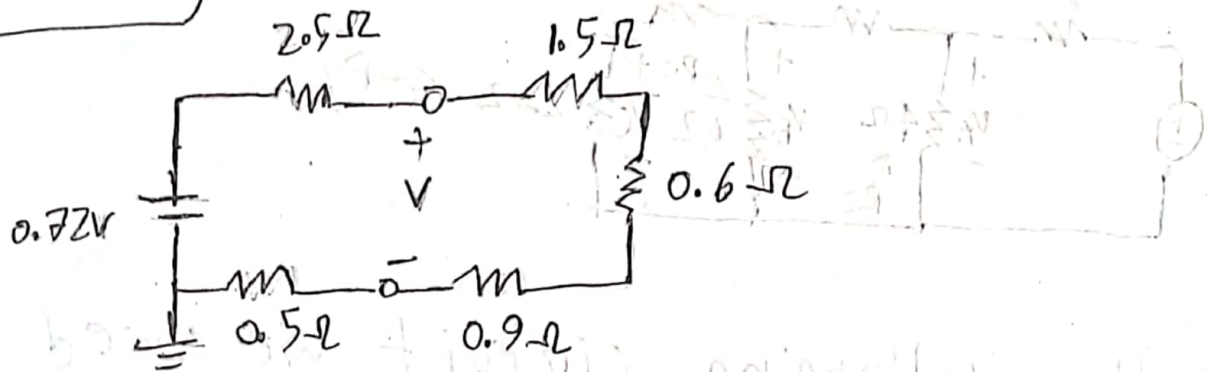

we can draw the following circuit as

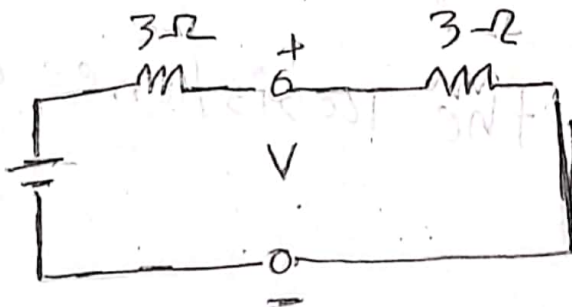


If we use voltage division rule we get

$$V = \frac{3}{3+3} \times 0.72V = 0.36V$$

$$\therefore V = 0.36V$$

Problem 8

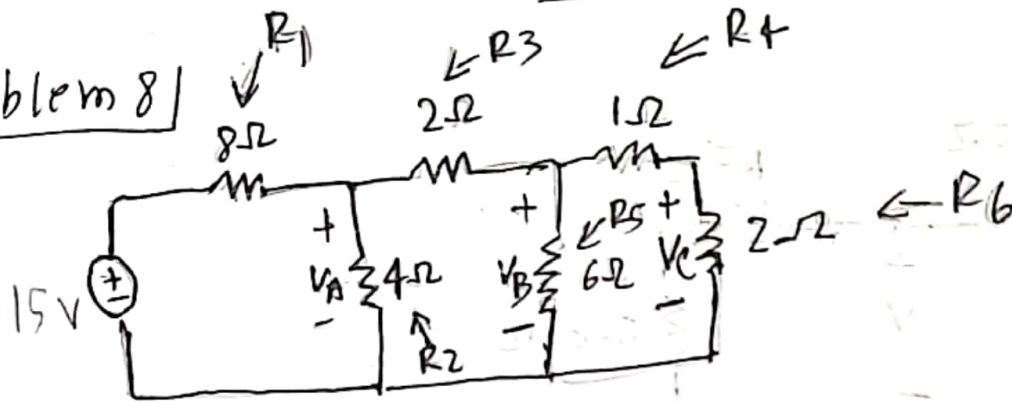

For the following circuit we need
to compute V_A at first, for this
we need to get the resistance of
 V_A .

$$R_{46} = R_4 + R_6 = 1 + 2 = 3\Omega$$

For, R_{456} we get,

$$\frac{1}{R_{456}} = \frac{1}{R_{46}} + \frac{1}{R_5}$$

$$= \frac{1}{3} + \frac{1}{6}$$


$$R_{456} = 2\Omega \quad \text{--- (1)}$$

$$R_{3456} = R_3 + R_{456} = 2 + 2 = 4\Omega$$

Again,

$$\begin{aligned} \frac{1}{R_{23456}} &= \frac{1}{R_{3456}} + \frac{1}{R_5} \\ &= \frac{1}{4} + \frac{1}{4} \\ &= 2\Omega \end{aligned}$$

Now, the circuit looks,

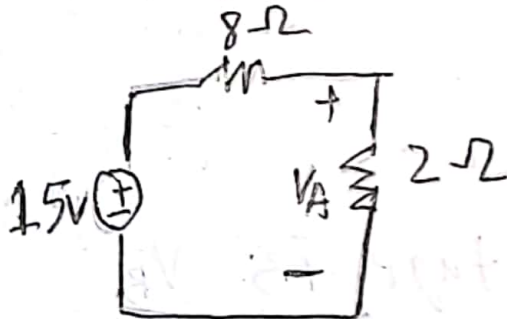

$$\begin{aligned} \therefore V_A &= \frac{R_{23456}}{R_1 + R_{23456}} \times V_{eq} \\ &= \frac{2}{8 + 2} \times 15 \\ &= 3V \end{aligned}$$

From equation ① we get,

$$R_{456} = 2\Omega$$

For V_B the equivalent voltage is V_A .

$$\therefore V_B = \frac{R_3}{R_3 + R_{456}} \times V_A$$

$$= \frac{2}{2 + 2} \times 3$$

$$= 1.5 \text{ V}$$

For V_C the equivalent voltage is V_B


$$\therefore V_C = \frac{R_6}{R_6 + R_4} \times V_B$$

$$= \frac{2}{2 + 1} \times 1.5$$

$$= 1 \text{ V}$$

Slide - 4

Problem - 9

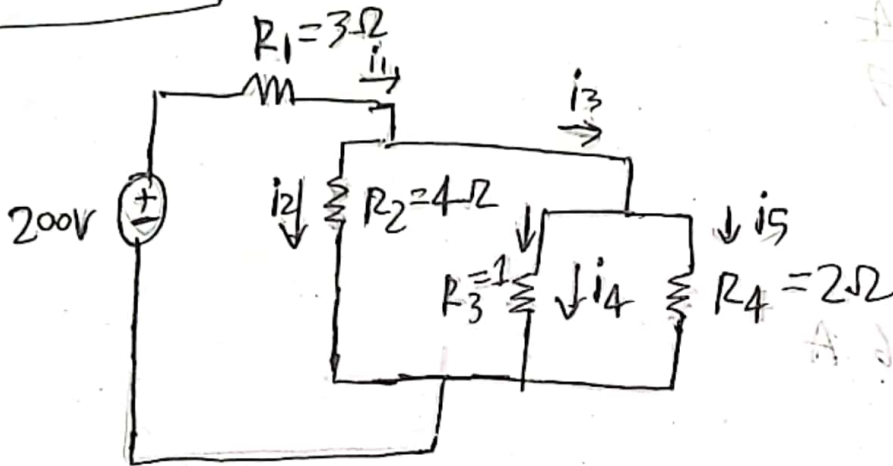

Here,

$$\frac{1}{R_{34}} = \frac{1}{R_3} + \frac{1}{R_4}$$

$$\Rightarrow \frac{1}{R_{34}} = \frac{1}{1} + \frac{1}{2}$$

$$\therefore R_{34} = \frac{2}{3} \Omega \quad \text{--- (1)}$$

Again,

$$\frac{1}{R_{234}} = \frac{1}{R_2} + \frac{1}{R_{34}}$$

$$= \frac{1}{4} + \frac{1}{2/3}$$

$$\therefore R_{234} = \frac{4}{7} \Omega \quad \text{--- (2)}$$

$$\begin{aligned}\therefore R_{1234} &= R_1 + R_{234} \\ &= 3 + \frac{4}{7} \\ &= \frac{25}{7}\end{aligned}$$

$$i_1 = \frac{200}{25/7} = 56 \text{ A}$$

For other i_2, i_3, i_4 is we need to use current division rule.

From eq (ii) we get, and from eq (i)

$$R_{234} = \frac{4}{7}, \quad R_{34} = \frac{2}{3}$$

$$\begin{aligned}\therefore i_2 &= \frac{R_{234}}{R_2} \times i_1 \\ &= \frac{4/7}{4} \times 56 \\ &= 8 \text{ A}\end{aligned}$$

$$i_3 = \frac{R_{234}}{R_{34}} \times i_1$$

$$= \frac{4/7}{2/3} \times 56$$

$$= 48 \text{ A}$$

$$i_4 = \frac{R_{34}}{R_3} \times i_3$$

$$= \frac{2}{3} \times 48$$

$$= 32 \text{ A}$$

$$i_5 = \frac{R_{34}}{R_4} \times i_3$$

$$= \frac{2/3}{2} \times 48$$

$$= 16 \text{ A}$$



$$\frac{1}{5.8} + \frac{1}{1.9} =$$

$$\frac{1}{0.1} + \frac{1}{0.1} =$$

$$2 \times 0.5 =$$

$$\frac{1}{0.4} + \frac{1}{5.4} =$$

$$\frac{1}{0.5} + \frac{1}{0.5} =$$

$$2 \times 1 =$$