

CSE-250

Simulation Project

Name: MD Ikramul Kayes


ID : 21301576

Sec : 07

Group : 05

Methodology

Getting values of
unknown variables

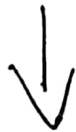

Putting them on
Lt spice



Use specific commands



Plot them accordingly



Use specific commands
using Lt spice plot

Question 2

① Ans: As my student ID is 21301576

charging or Discharging time is

$$5\tau = 2+1+3+0+1+5+7+6$$

$$\Rightarrow \tau = \frac{25}{5} \times 10^{-3}$$

$$= 5 \times 10^{-3}$$

we know,

$$\tau = RC = \tau$$

$$\Rightarrow R = \frac{5 \times 10^{-3}}{2 \times 10^{-6}} = 2.5 \times 10^3$$


Lets assume, $R = R_1 + R_2 + R_3$

$$\therefore R_{eq} = R + R \parallel R$$

$$= \frac{3}{2} R$$

$$\therefore \frac{3}{2} R = 2.5 \times 10^3$$


$$\therefore R = 1.67 \times 10^3$$

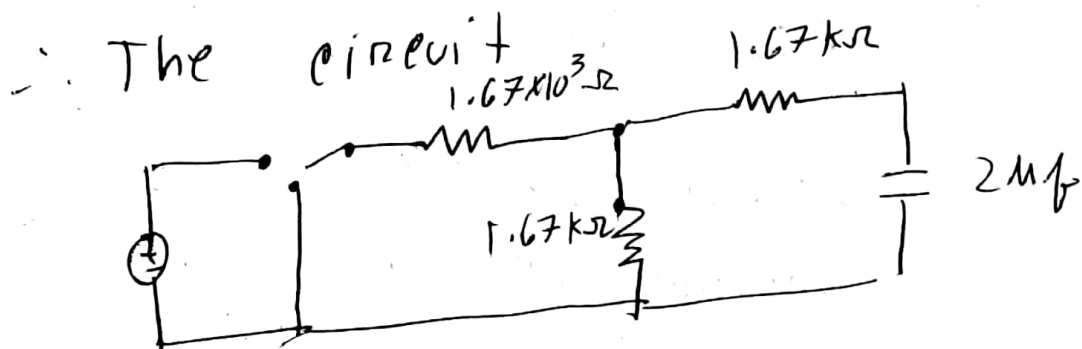

(ii) As the ^{highest} ~~final~~ voltage of the following plot is 5V, so the total voltage for the circuit will be $2 \times 5V$, which is 10V. As in 10V the full cycle will be complete. As in 5V it only complete half cycle.

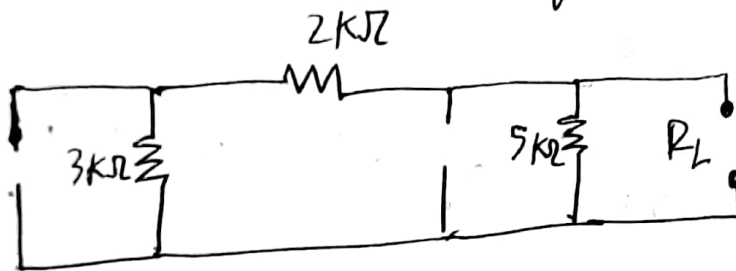Question 2)

① The following circuit can be drawn as
for the value of R_L



$$\therefore R_L = 5 \parallel (2 + 3) \parallel 5$$
$$= 2.5 \text{ k}\Omega$$

② ~~P_t~~ As my ID is 21301576

$$\therefore P_{\max} = 2 + 1 + 3 + 0 + 1 + 5 + 7 + 6$$
$$= 25 \text{ mW}$$

$$\text{As, } P_{\max} = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 \times R_L$$

For, P_{max} $R_L = R_{th}$

~~$\Rightarrow V_{th} =$~~

$$\Rightarrow P_{max} = \frac{(V_{th})^2}{(2.5 + 2.5) \times 10^3} \times (2.5) \times 10^3$$


$$\Rightarrow V_{th} = 15.811$$

(iii) The I_s we get for the circuit


is 0.00364 A or 3.64 mA

(iv) As, I am seeing the max power generated by thevenin and original circuit is same, so the thevenin circuit is correct.

Question
1(3)ans:

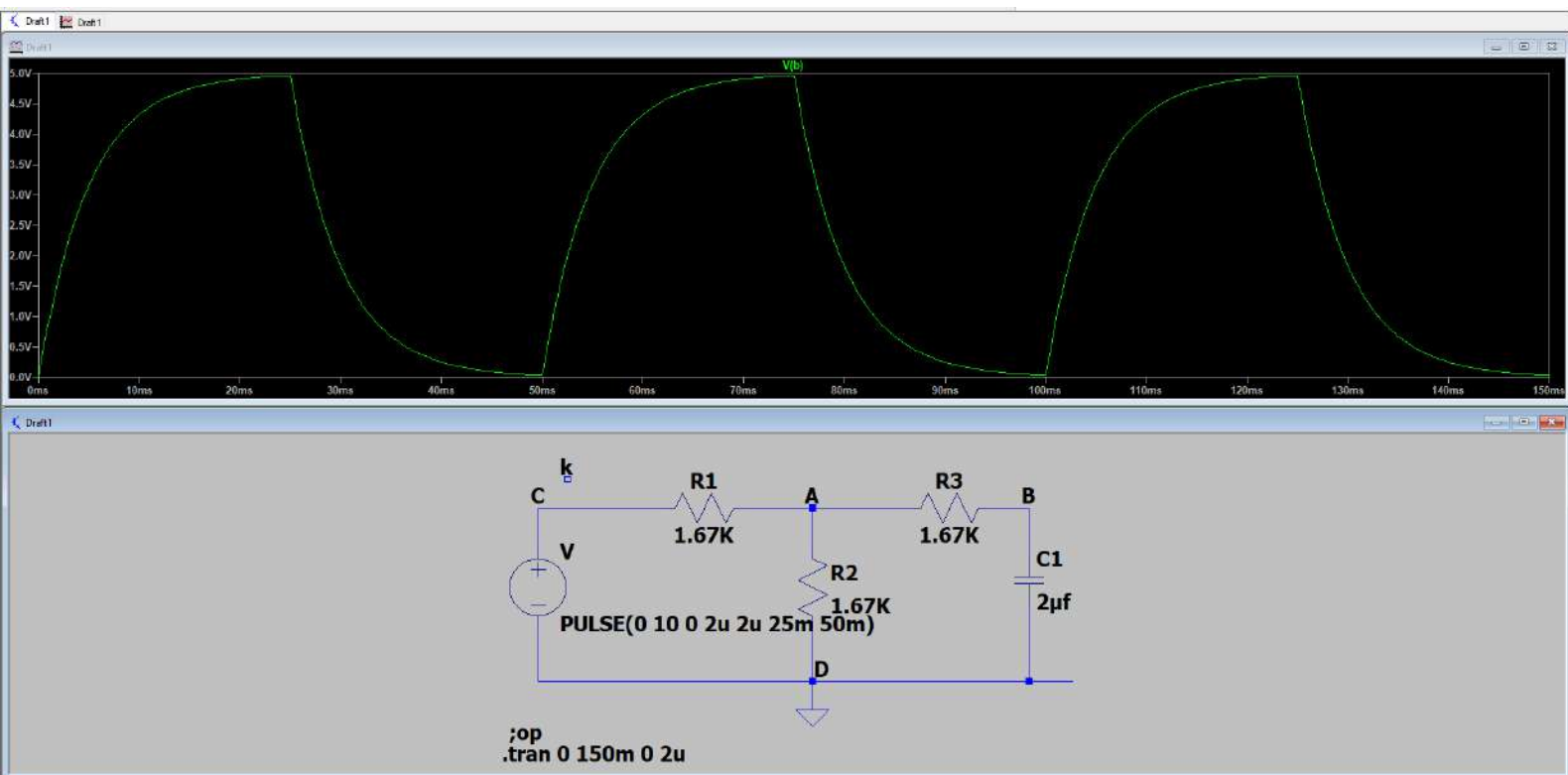

Question
2(2) ans:

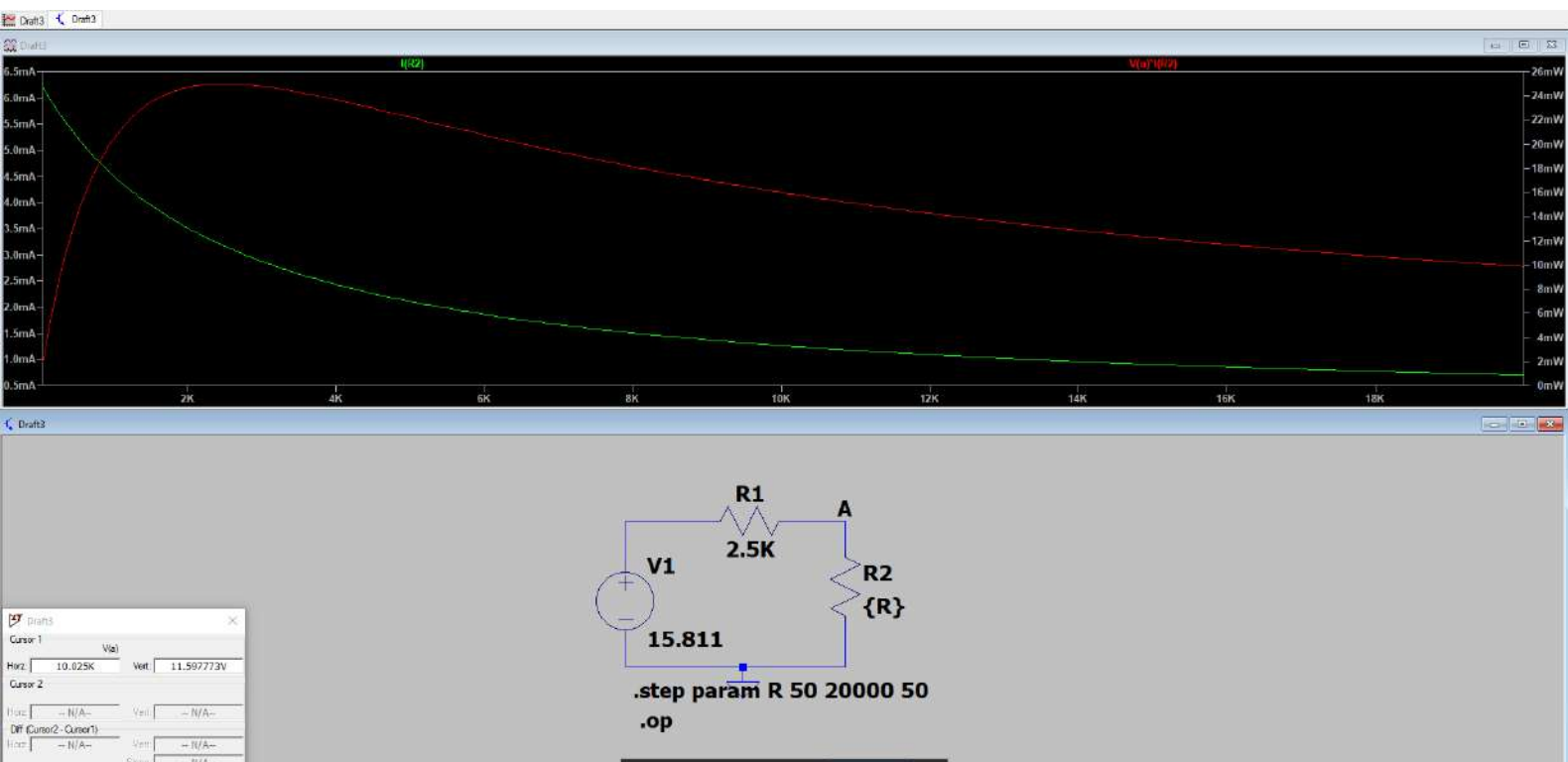

Question
2(4)ans:

