

CSE-250


Assignment - 04

Name: MD Ikramul Kayes

ID : 21301576

Sec : 07

Problem 2

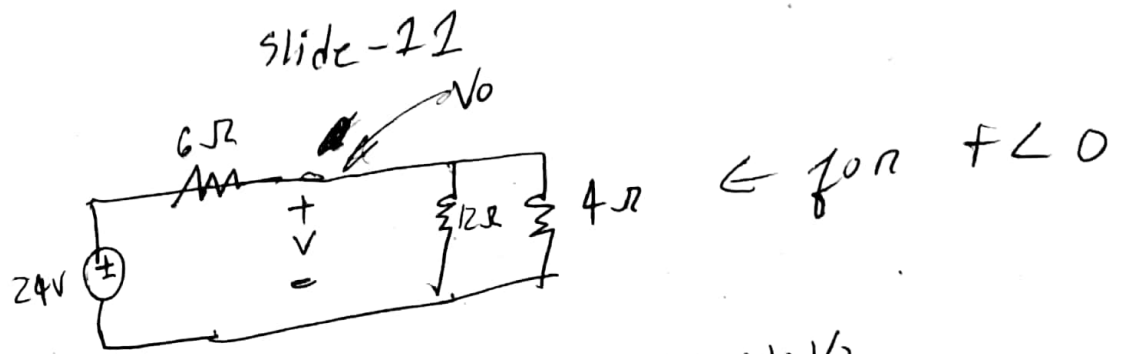


$$-24 + 6i + 3i = 0$$

$$\therefore i = 2.67 \text{ A}$$

$$\begin{cases} -24 + 6 \times 2.67 + v_o \\ \therefore v_o = 8 \end{cases}$$

for $t > 0$,

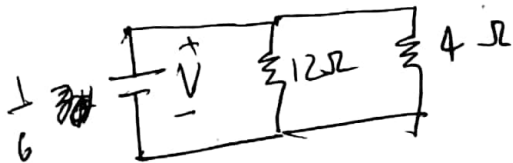

$$R_{eq} = 12 \parallel 4 = 3$$

$$\tau = RC = 3 \times \frac{1}{6} = \frac{1}{2} \text{ sec}$$

~~or~~

$$\Rightarrow v_c = v_o e^{-t/\tau}$$

$$\therefore v_c = 8 e^{-t/\tau} \text{ V}$$


$$\therefore w_c = \frac{1}{2} C v_o^2$$

$$= \frac{1}{2} \times \frac{1}{6} \times (8)^2$$

$$= 5.333 \text{ J (Ans)}$$


Problem-3

For $t < 0$,

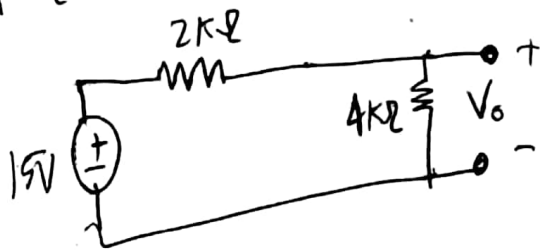

$$V_0 = \frac{4}{2+4} \times 15 = 10V$$

For $t > 0$,

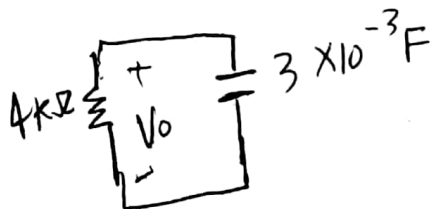

$$\tau = RC = 4 \times 10^3 \times 3 \times 10^{-3} = 12 \text{ sec}$$

$$V_c = V_0 e^{-t/\tau}$$

$$V_c = 10 e^{-t/12}$$

Problem 4)

$$a) i = \frac{V}{R}$$

$$\Rightarrow R = \frac{V}{i}$$

$$= \frac{10e^{-4t}}{0.2e^{-4t}} = 50$$

$$\tau = RC$$

$$\Rightarrow C = \frac{\tau}{R} = \frac{\frac{1}{4}}{50} = 5 \times 10^{-3} \text{ F}$$

$$b) \tau = \frac{1}{4} = 0.25 \text{ sec}$$

$$c) w_E(0) = \frac{1}{2} C V_0^2 = \frac{1}{2} \times 5 \times 10^{-3} \times (10)^2$$
$$= 0.25 \text{ J}$$

$$d) w = \frac{1}{2} C V_0^2 (1 - e^{-2t/\tau})$$


$$\Rightarrow 0.25 \times \frac{50}{100} = \frac{1}{2} \times 5 \times 10^{-3} \times (10)^2 \times (1 - e^{-\frac{2t}{0.25}})$$

$$\Rightarrow e^{-2t/\tau} = 0.5$$

$$\Rightarrow t = 0.0866$$
$$= 86 \text{ ms}$$

Problem 5


$t < 0$

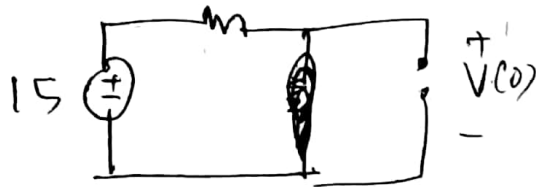

Here, we can easily

say $V(0) = 15$

~~$t > 0$~~ $t > 0$,

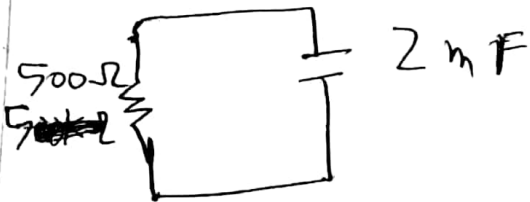

Here,

$$\tau = RC$$


$$= 500 \times 10^3 \times 2 \times 10^{-3}$$

$$= 1000 \text{ s}$$

$$V(t) = 15 e^{-t/\tau}$$

$$\therefore V(t) = 15 e^{-t/1000}$$

for $t > 1$,

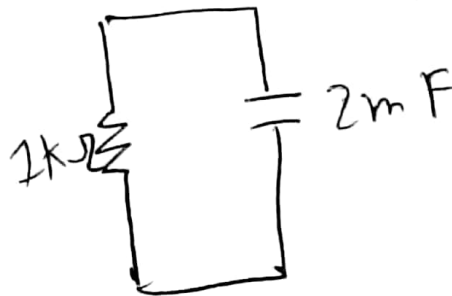

we got previously,

$$V_0(t) = 15 e^{-\frac{t-1}{\tau}}$$

$$V_0(1) = 5.518$$

$$V = V_0 e^{-\frac{(t-t_0)}{\tau}}$$


$$\therefore V(t) = 5.518 e^{-\frac{1}{2}(t-1)}$$

$$\tau = R C$$

$$= 1 \times 10^3 + 2 \times 10^{-3}$$

$$= 2 \text{ sec}$$

Problem 6

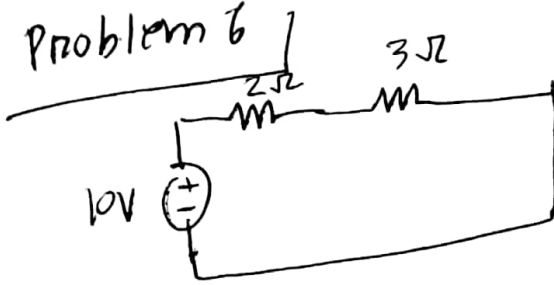

For $t < 0$

Here,


$$5i = 10$$

$$\therefore i = 2A$$

$$i_0 = 0$$

$$\therefore V_0 = \frac{3}{3+2} \times 10 = 6V$$

For $t > 0$

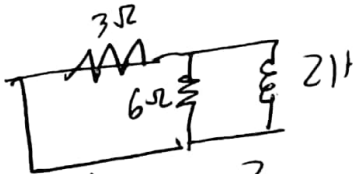

$$R_{eq} = 3 \parallel 6 = 2\Omega$$

$$\tau = \frac{L}{R_{eq}} = \frac{2}{2} = 1 \text{ sec}$$

$$\therefore i(t) = i e^{-t/\tau} = 2e^{-t}$$

$$\begin{aligned} V_0(t) &= iR \\ &= 2 \times 2e^{-t} \\ &= 4e^{-t} \end{aligned}$$

$$\begin{aligned} i_0 &= \frac{R_{eq} \times 2e^{-t}}{R_1} \\ &= \frac{2}{6} \times 2e^{-t} \\ &= -\frac{2}{3} e^{-t} \end{aligned}$$

Problem 7

For $t < 0$




$$i = \frac{4 \parallel 2}{2} \times 24 = 16 \text{ A}$$

$$i_0 = 24 - 16 = 8 \text{ A}$$

$$\therefore V_0 = iR = 16 \times 2 = 32 \text{ V}$$

For $t > 0$

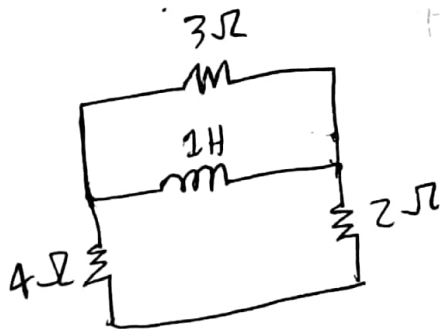

$$\tau = \frac{L}{R} = \frac{1}{2}$$

$$i(t) = i e^{-t/\tau} = 16 e^{-2t}$$

$$i_0 = \frac{-2}{6} \times 16 e^{-2t} = -5.333 e^{-2t}$$

$$\begin{aligned} V_0 &= i R = 5.333 e^{-2t} \times 2 \\ &= 10.667 e^{-2t} \end{aligned}$$

$$\therefore v(t) = 5.518 e^{-\frac{1}{2}(t-1)}$$

Problem - 8]

a) we know,

$$\tau = \frac{L}{R}$$

$$= \frac{L}{\frac{V_i}{i}} = \frac{L}{\frac{90e^{-50t}}{30/e^{-50t}}} = \frac{L}{3}$$

$$\therefore L = 3\tau$$

$$= 3 \times \frac{1}{50}$$

$$= 0.06$$

$$\therefore L = 60 \text{ mH}$$

$$\text{Also, } R = \frac{V}{i} = \frac{90 e^{-50t}}{30 e^{-50t}} = 3 \Omega$$

b) we know,

$$V(t) = 90 e^{-\frac{t}{\tau}}$$

if we compare the equation with $V = 90 e^{-\frac{t}{\tau}}$


$$\therefore \tau = \frac{1}{50} = 0.02 \text{ sec}$$

$$\begin{aligned} \text{c) we know, } W_0 &= \frac{1}{2} L i_0^2 \\ &= \frac{1}{2} \times 60 \times 10^{-3} (30)^2 \\ &= 27 \text{ J} \end{aligned}$$

$$\begin{aligned} \text{d) we know, } W_R(t) &= \frac{1}{2} L i^2 (1 - e^{-2t/\tau}) \\ &= 6.2786 \end{aligned}$$

$$\begin{aligned} \therefore \text{fraction of energy is } (100 - W_R(t)) \\ = 93.72 \end{aligned}$$

Problem 9

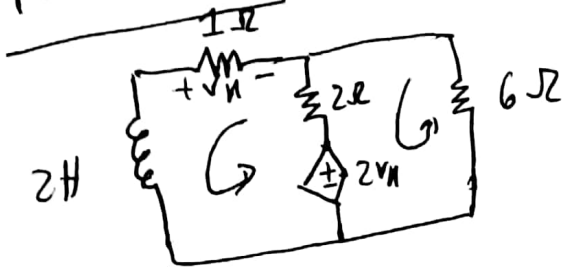

$$V_1 = -i$$

$$\Rightarrow -V_1 + L \frac{di_1}{dt} - 2V_1 + 2(i_1 - i_2) = 0$$

$$\Rightarrow i_1 + 2 \frac{di_1}{dt} + 2i_1 + 2i_1 - 2i_2 = 0$$

$$\Rightarrow 5i_1 + 2 \frac{di_1}{dt} - 2i_2 = 0 \quad \text{--- (1)}$$

also,

$$6i_2 + 2(i_2 - i_1) + 2V_1 = 0$$

$$\Rightarrow 6i_2 + 2i_2 - 2i_1 - 2i_1 = 0$$

$$\Rightarrow 2i_2 = i_1$$

$$\therefore i_2 = 0.5i_1$$

Putting i_2 in eq (1),

$$\Rightarrow 5i_1 + 2 \frac{di_1}{dt} - i_1 = 0$$

$$\Rightarrow \frac{di_1}{dt} = -2i_1$$

$$\therefore \int \frac{di_1}{i_1} = \int -2 dt$$

$$\Rightarrow \ln(i_1) = -2t + C$$

$$\Rightarrow i_1 = e^{-2t + C}$$

$$= C_2 e^{-2t}$$

$$\therefore i(0) = \cancel{7} C_0 e^{-2 \times 0}$$

$$[\text{As } i(0) = 7]$$

$$\Rightarrow 7 = C_0$$

$$\therefore i(t) = 7e^{-2t}$$

$$\therefore v_R = -i$$


$$= -7e^{-2t}$$

Problem 12

$$= -7e^{-2t}$$


Problem 12

$t < 0$

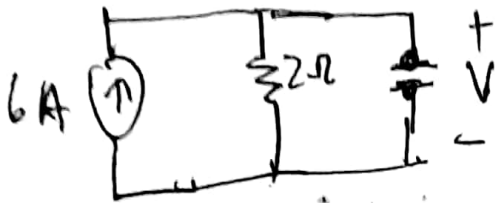


$$V_0 = 6 \times 2 = 12V$$

$t > 0$

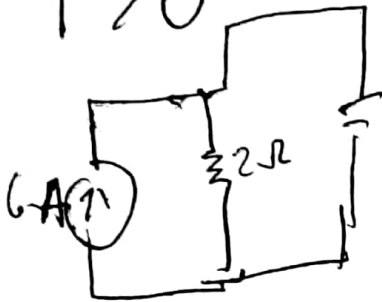


$$V(t) = 6 \times 2 = 12V$$

Problem-13

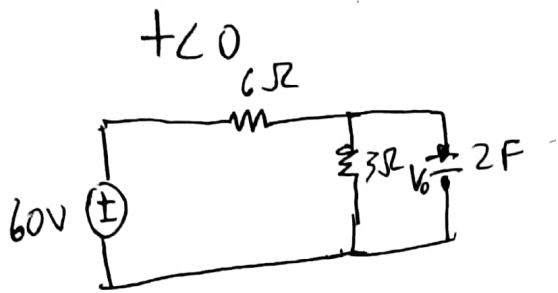

$$V_0 = \frac{3}{3+6} \times 60 = 20V$$

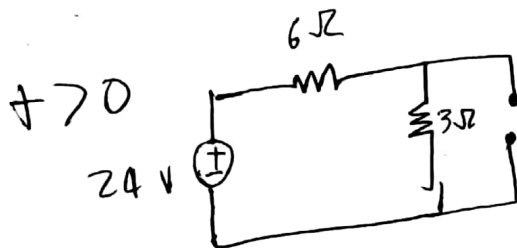

$$\tau = 3/6 \times 2 = 1$$

$$V(\infty) = \frac{3}{6+3} \times 24 = 8V$$

$$V(t) = V(\infty) + [V(0) - V(\infty)]e^{-t/\tau}$$

$$= 8 + (20 - 8)e^{-t/1}$$


$$= 8 + 12e^{-t/1}$$

$$i(t) = C \frac{dV}{dt}$$

$$= 2 \times \left(0 - \frac{12}{1} e^{-t/1} \right)$$

$$= -24e^{-t/1}$$

Prob-14) For $t < 0$

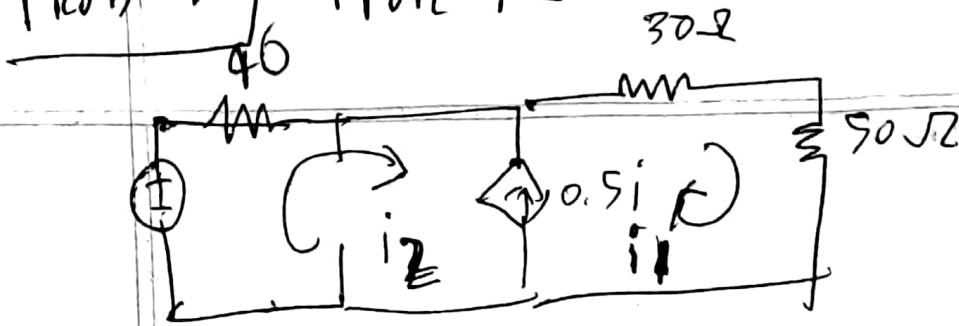

$$-80 + 40i_2 + 30i_1 + 50i_1 = 0$$

$$\Rightarrow 80i_1 + 40i_2 = 80 \quad \text{--- (1)}$$

$$i_1 - i_2 = 0.5i_1$$


$$\Rightarrow 0.5i_1 - i_2 = 0 \quad \text{--- (2)}$$

Solving eq (1) (2) we get

$$i_1 = 0.8, i_2 = 0.4$$

$$i(0) = 0.8$$

For $t > 0$

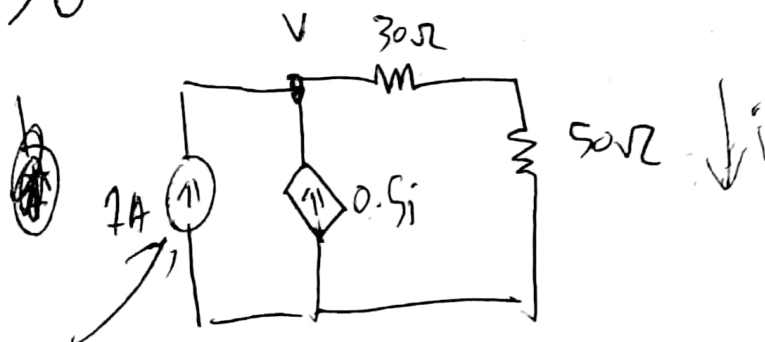

dummy source

$$i = \frac{V}{80}$$

$$V\left(\frac{1}{80}\right) - 1 - \frac{V}{80} \times 0.5 = 0$$

$$V = 160 \text{ V}$$

$$R = \frac{V}{i} = \frac{160}{1} = 160 \Omega$$

$$\tau = RC = 160 \times 3 = 480 \text{ sec}$$

$$i(t) = i(\infty)$$

$$\text{Also, } i(\infty) = 0$$

$$\Rightarrow i(t) = i(\infty) + [i(0) - i(\infty)] e^{-t/\tau}$$

$$\therefore i(t) = +0.8 e^{-t/480}$$

problem 15/

Prob 15)

① Ans: The time constant of a circuit is the time required the response to decay to a factor of $1/e$ or 36.8% of its initial value.

② Given,

$$5\tau = 45 \times 10^{-3} \text{ sec} \quad \leftarrow \text{Total time}$$

$$\Rightarrow \tau = \cancel{9 \text{ sec}} \quad 9 \times 10^{-3} \text{ sec}$$

③ Given, $V(\infty) = 6V$

$$V(0) = -2V$$

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}$$

$$= 6 + [-2 - 6] e^{-t/9 \times 10^{-3}}$$

$$= 6 - 8e^{-\frac{1000t}{9}}$$

IV) We know, $W_0 = \frac{1}{2} C V_0^2$

~~or~~

Hence,


$$\tau = RC$$

$$\Rightarrow C = \frac{9 \times 10^{-3}}{4 \times 10^3} = 2.25 \times 10^{-6}$$


$$\therefore W_0 = \frac{1}{2} C V_0^2$$

$$= \frac{1}{2} \times 2.25 \times 10^{-6} \times (-2)^2$$

$$= 4.5 \times 10^{-6} \text{ J}$$

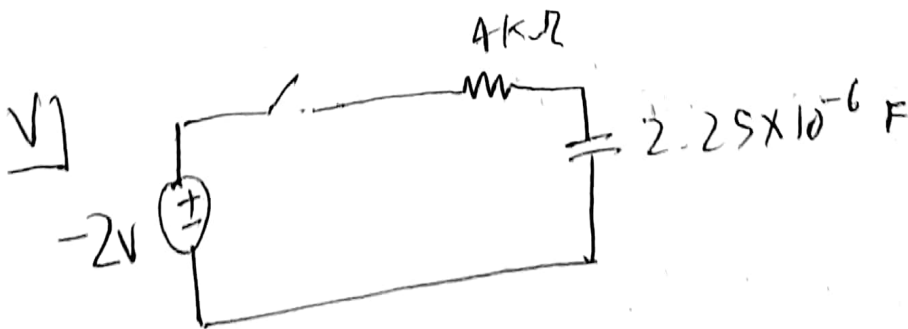

Problem 16

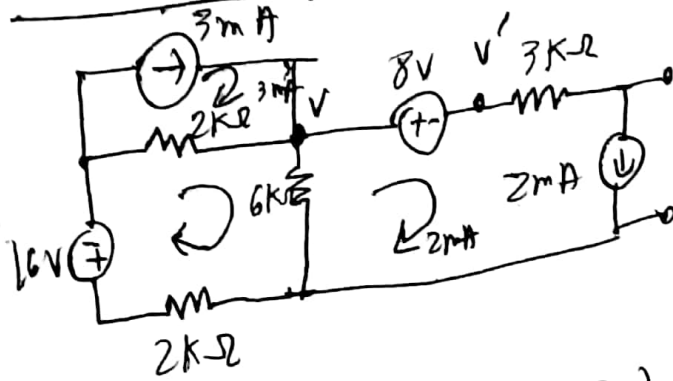

$$2i + 16 + 2(i - 3) + 6(i - 2) = 0$$

$$\Rightarrow 10i = 2$$

$$\therefore i = 0.2$$

$$V - 0 = 6(i - 2)$$

$$\Rightarrow V = 6(0.2 - 2) \\ = -10.8$$

Also,


$$V - V' = 8$$

$$\Rightarrow V' = V - 8 \\ = -10.8 - 8 \\ = -18.8$$

$$V' - V_{th} = 3 \times 2$$

$$\Rightarrow V_{th} = -18.8 - 6 = -24.8$$

for R_{th} ,

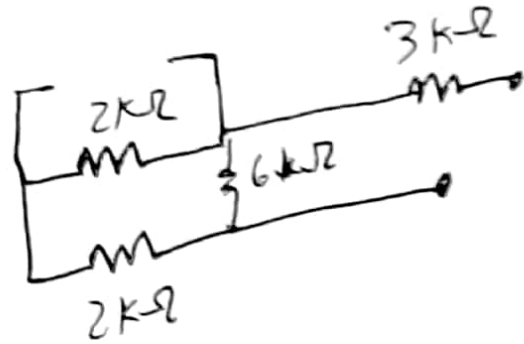

$$R_{th} = (4 || 6 + 3) = 5.4 \text{ k}\Omega$$

$$\tau = RC = 5.4 \times 10^3 \times 1 \times 10^{-6}$$

$$= 5.4 \text{ ms}$$

$$V(t) = -24.5 + 24.5 e^{-t/(5.4 \times 10^{-3})}$$

$$i(t) = C \frac{\partial V}{\partial t} = 1 \times 10^{-6} \times \left(-\frac{24.5}{5.4 \times 10^{-3}} e^{-\frac{t}{5.4 \times 10^{-3}}} \right) \times 10^3$$


$$= 4.59 e^{-\frac{t}{5.4 \times 10^{-3}}}$$

④ ~~$\tau = 9 \text{ ms}$~~ from

~~④~~

Problem 17


We can

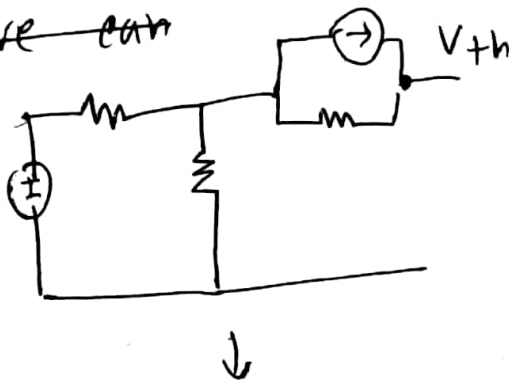

From the circuit we can say
the V_{th} is 20 V


$$\therefore V_{th} = 20 \text{ V}$$

For R_{th}

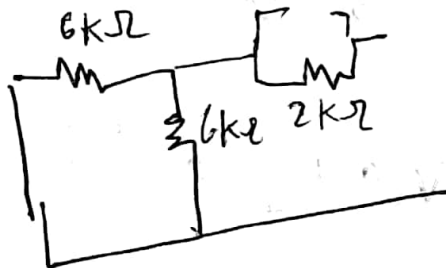

$$R_{th} = 2 + (6 \parallel 6) \\ = 5 \text{ k}\Omega$$

Thevenin circuit

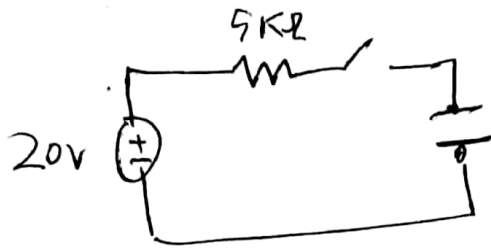


For

$t < 0$,



$$\therefore V(0) = 0$$

For $t > 0$,

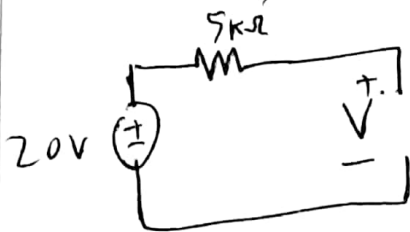

$$V(\infty) = 20V$$

$$\tau = RC = 5 \times 10^3 \times 100 \times 10^{-6} = 0.5 \text{ sec}$$

$$V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}$$

$$= 20 + 20e^{-t/0.5}$$

$$= 20 - 20e^{-t/0.5}$$


$$i(t) = 4.59 e^{-\frac{t}{5.4 \times 10^{-3}}}$$

$$= 4.59 e^{-\frac{t}{5.4 \times 10^{-3}}}$$

Problem 18


Problem 18

$t < 0$

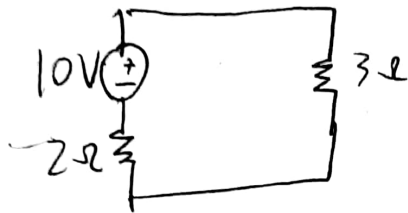

$$i_0 = 2 \text{ A}$$

$t > 0$

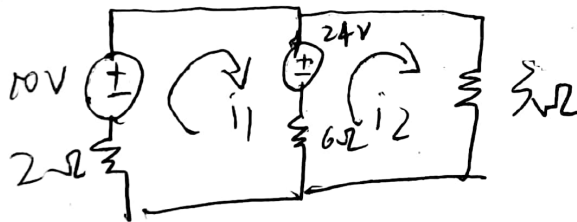

$$2i_1 - 10 + 24 + 6(i_1 - i_2)$$

$$\Rightarrow 8i_1 - 6i_2 = -14 \quad \text{--- (I)}$$

$$3i_2 + 6(i_2 - i_1) - 24 = 0$$

$$\Rightarrow -6i_1 + 9i_2 = 24 \quad \text{--- (II)}$$

Solving eq (I) and (II) we get,

$$i_1 = 0.5, \quad i_2 = 3$$

$$\text{Here, } i(\infty) = i_2 = 3$$

For R_{eq}



$$R_{eq} = 6 \parallel 2 + 3$$

$$= 4.5$$


$$\tau = \frac{L}{R} = \frac{2}{4.5} = \frac{4}{9}$$

$$i(k) = i(\infty) + (i(0) - i(\infty))e^{-\frac{t}{\tau}}$$

$$= 3 + (2 - 3)e^{-\frac{2}{4}t}$$

$$= 3 - e^{-\frac{2}{4}t}$$

Problem 19)

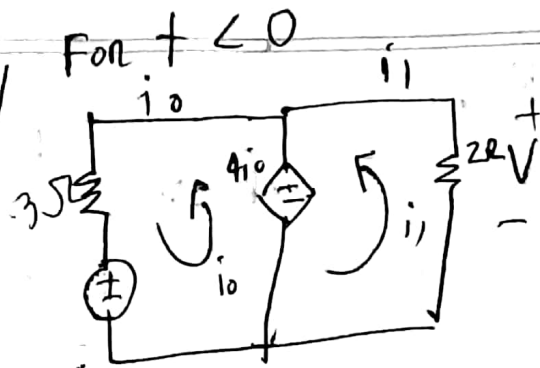

$$3i_o + 24 - 4i_o = 0 \quad \text{--- (I)}$$

$$4i_o + 2i_1 = 0 \quad \text{--- (II)}$$

Solving equation (I), (II) we get,

$$i_o = 24$$

$$i_1 = -2i_o = -48$$


$$V(t) = -2 \times -48 = 96 \text{ V}$$

$t > 0$,

Here, $i_o = 0$, so ~~4i_o~~ $4i_o = 0$,

The circuit can be drawn

For ~~P_{avg}~~ P_{avg} ,

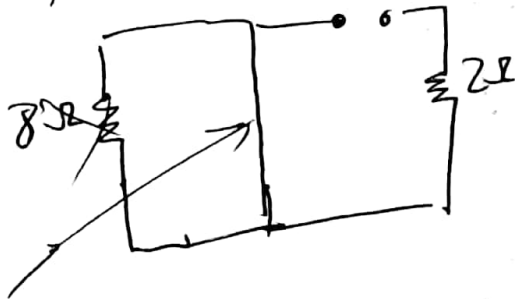

As $i_o = 0$, so $4i_o = 0$


~~P_{avg}~~ $P_{eq} = 2\Omega$

$$\tau = \frac{L}{R}$$

$$= \frac{0.5}{2}$$

$$= 0.25 \text{ sec}$$

For $V(\infty)$

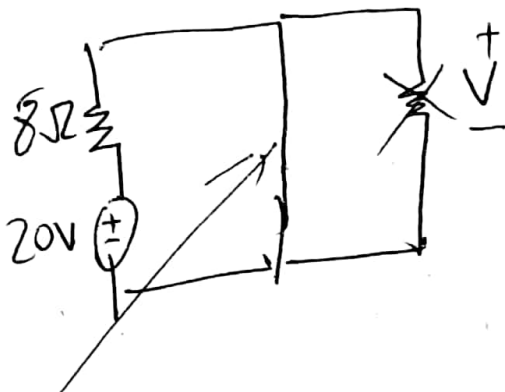

As $i_o = 0$, so $4i_o = 0$

~~$V(\infty)$~~

$$\therefore V(\infty) = 0$$

$$\therefore V(t) = V(\infty) + [V(0) - V(\infty)] e^{-t/\tau}$$



~~$$= 0 + [96 - 0] e^{-4t}$$~~

$$= 0 + [96 - 0] e^{-\frac{t}{0.25}}$$

$$= 96 e^{-4t} \quad (\text{Ans})$$


Problem 20

when $t < 0$

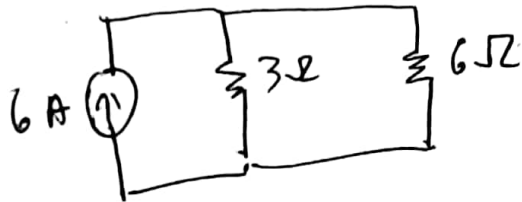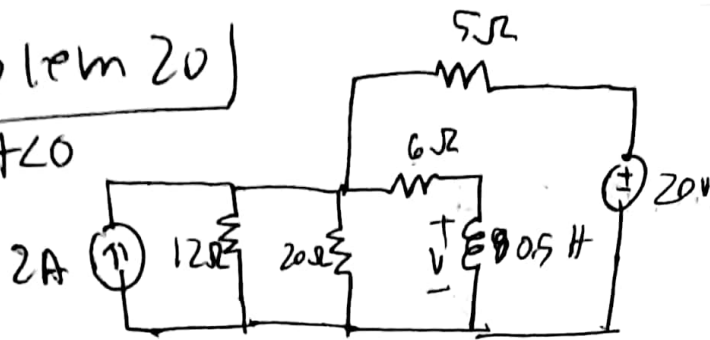


$$i(0) = \frac{3}{3+6} \times 6$$

$$i(0) = 2A$$

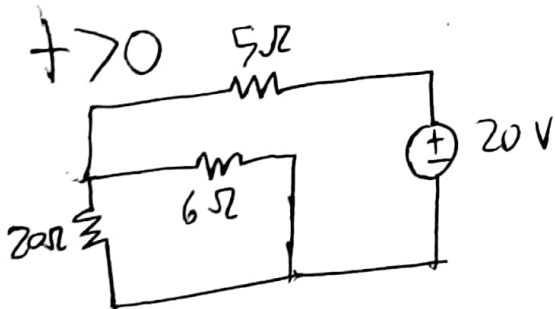

can be drawn as,

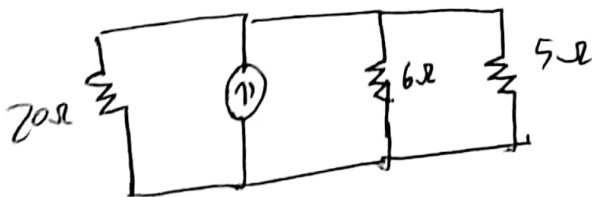

$$i(\infty) = \frac{20 \parallel 6 \parallel 5}{6} \times 4$$

$$\therefore i(\infty) = 1.6A$$

~~Req = 6 + (20 || 5)~~

$$R_{eq} = 6 + (20 \parallel 5)$$

$$= 10\Omega$$

$$\therefore \tau = \frac{L}{R} = \frac{0.5}{10} = 0.05 \text{ sec}$$

$$i(t) = i(\infty) + [i(0) - i(\infty)]e^{-\frac{t}{\tau}}$$

$$= 1.6 + (2 - 1.6)e^{-\frac{t}{0.05}}$$

$$\therefore i(t) = 1.6 + 0.4e^{-\frac{t}{0.05}}$$

$$\therefore V(t) = L \frac{di}{dt}$$


$$= 0.5 \left(0 + \frac{-0.4}{0.05} e^{-\frac{t}{0.05}} \right)$$

$$\therefore V(t) = -4e^{-20t}$$

Prob-21

$$R_{eq} = 2.4$$


+ < 0

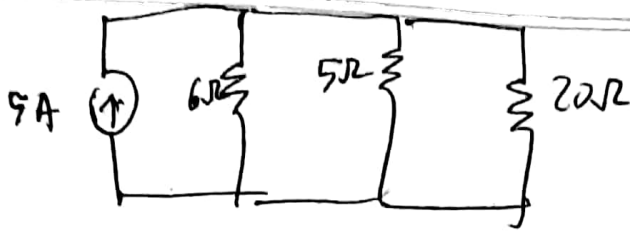

$$i_1(0) = \frac{2.4}{5} \times 5 = 2.4$$

$$i_2(0) = \frac{2.4}{20} \times 5 = 0.6$$

+ > 0

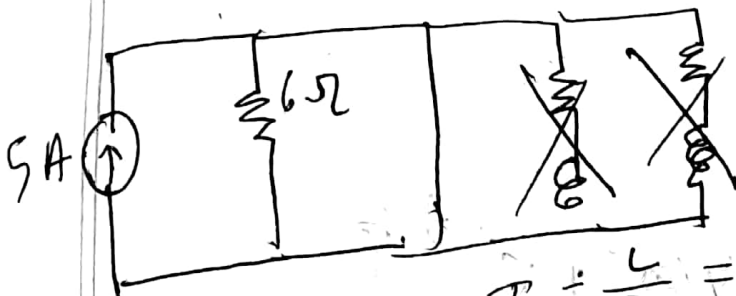

$$i_1(\infty) = 0 \rightarrow \tau_1 = \frac{L}{R} = \frac{2.5}{5} = 0.5$$

$$i_2(\infty) = 0 \rightarrow \tau_2 = \frac{L}{R} = \frac{4}{20} = 0.2$$

$$i_1(t) = i_1(\infty) + [i_1(0) - i_1(\infty)] e^{-\frac{t}{\tau_1}}$$

$$= 2.4 e^{-2t}$$

$$i_2(t) = i_2(\infty) + [i_2(0) - i_2(\infty)] e^{-\frac{t}{\tau_2}}$$

$$= 0.6 e^{-5t}$$